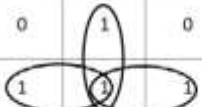


Answers

Answer 1

4(a)	$X = ((P \text{ XOR } Q) \text{ XOR } R)$ $Y = ((P \text{ XOR } Q) \text{ AND } R) \text{ OR } (P \text{ AND } Q)$ or $X = (\overline{P.Q + P.Q}) . R + (\overline{P.Q + P.Q}) . \overline{R}$ $Y = (\overline{P.Q + P.Q}) . R + P.Q$ One mark for correct use of XOR One mark for correct use of AND One mark for correct use of OR One mark for X correct One mark for Y correct	5
4(b)(i)	X: Sum Y: Carry (out)	2
4(b)(ii)	Carry (in)	1

Answer 2

4(a)	<p>For each expression, 2 marks all products correct no incorrect products seen, 1 mark 2 or 3 products correct, max 4</p> <p>$X = \overline{A} . \overline{B} . C + \overline{A} . B . \overline{C} + A . \overline{B} . \overline{C} + A . B . C$</p> <p>$Y = \overline{A} . B . C + A . \overline{B} . C + A . B . \overline{C} + A . B . C$</p>	4																														
4(b)	<p>One mark for each correct K-map max 2</p> <div><div><p>OUTPUT X AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td></tr></table></div><div><p>OUTPUT Y AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr></table></div></div>		00	01	11	10	0	0	1	0	1	1	1	0	1	0		00	01	11	10	0	0	0	1	0	1	0	1	1	1	2
	00	01	11	10																												
0	0	1	0	1																												
1	1	0	1	0																												
	00	01	11	10																												
0	0	0	1	0																												
1	0	1	1	1																												
4(c)(i)	<p>One mark for OUTPUT X no loops</p> <p>OUTPUT Y one mark vertical loop correct one mark horizontal loops correct</p> <div><div><p>OUTPUT X AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td></tr></table></div><div><p>OUTPUT Y AB</p><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr></table></div></div>		00	01	11	10	0	0	1	0	1	1	1	0	1	0		00	01	11	10	0	0	0	1	0	1	0	1	1	1	3
	00	01	11	10																												
0	0	1	0	1																												
1	1	0	1	0																												
	00	01	11	10																												
0	0	0	1	0																												
1	0	1	1	1																												

4(c)(ii)	One mark for each correct product and no incorrect products max 3 $A.B + B.C + A.C$	3
4(d)	Logic circuit: Full Adder X: Sum Y: Carry	3

Answer 3

4(a)	For X 1 mark for all products correct For Y 2 marks for 3 products correct, no other products seen $X = \bar{A}.\bar{B}.\bar{C} + A.B.C$ $Y = \bar{A}.B.C + A.\bar{B}.C + A.B.C$	3																											
4(b)	One mark for each correct K-map max 2 <div style="display: flex; justify-content: space-around; align-items: flex-start;"><div style="text-align: center;">OUTPUT X AB<table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table></div><div style="text-align: center;">OUTPUT Y AB<table><tr><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr></table></div></div>		00	01	11	10	0	1	0	0	0	1	0	0	1	0	00	01	11	10	0	0	0	0	0	1	1	1	2
	00	01	11	10																									
0	1	0	0	0																									
1	0	0	1	0																									
00	01	11	10																										
0	0	0	0																										
0	1	1	1																										
4(c)(i)	One mark for OUTPUT X no loops One mark for OUTPUT Y all loops correct and no others max 2 <div style="display: flex; justify-content: space-around; align-items: flex-start;"><div style="text-align: center;">OUTPUT X AB<table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table></div><div style="text-align: center;">OUTPUT Y AB<table><tr><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr></table></div></div>		00	01	11	10	0	1	0	0	0	1	0	0	1	0	00	01	11	10	0	0	0	0	0	1	1	1	2
	00	01	11	10																									
0	1	0	0	0																									
1	0	0	1	0																									
00	01	11	10																										
0	0	0	0																										
0	1	1	1																										
4(c)(ii)	One mark for each correct product $A.C + B.C$	2																											

Answer 4

5	(logic) Circuit // bi-stable Two Memory // data storage // registers // storing one bit of data JK/SR/D/T SR/JK/T/D	5
---	---	----------

Answer 5

3(a)	NOR	1																									
3(b)(i)	1 mark for X column, 1 mark for Y column <table><tr><td>A</td><td>B</td><td>Working Space</td><td>X</td><td>Y</td></tr><tr><td>0</td><td>0</td><td></td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td></td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td></td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td></td><td>1</td><td>0</td></tr></table>	A	B	Working Space	X	Y	0	0		0	0	0	1		0	1	1	0		0	1	1	1		1	0	2
A	B	Working Space	X	Y																							
0	0		0	0																							
0	1		0	1																							
1	0		0	1																							
1	1		1	0																							
3(b)(ii)	Half adder	1																									
3(b)(iii)	1 mark per bullet ∞ X is (used for) <u>carry</u> ∞ Y is (used for) <u>sum</u>	2																									
3(c)	1 mark per bullet for working (max 4) $\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D}$ $= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D}$ ∞ Adding in a second copy of the first term (Use of Idempotent Law) $= \bar{A}\bar{B}(\bar{C}\bar{D} + \bar{C}D + C\bar{D} + CD) + \bar{A}\bar{C}\bar{D}(B + \bar{B})$ ∞ Taking $\bar{A}\bar{B}$ and $\bar{A}\bar{C}\bar{D}$ outside brackets (Associative Law) $= \bar{A}\bar{B}(\bar{C}(\bar{D} + D) + C(\bar{D} + D)) + \bar{A}\bar{C}\bar{D}(B + \bar{B})$ ∞ Grouping $\bar{C}(\bar{D} + D) + C(\bar{D} + D)$ (Associative Law and Commutative Law) $= \bar{A}\bar{B}(\bar{C}(1) + C(1)) + \bar{A}\bar{C}\bar{D}(1)$ $= \bar{A}\bar{B}(\bar{C} + C) + \bar{A}\bar{C}\bar{D}(1)$ $= \bar{A}\bar{B}(1) + \bar{A}\bar{C}\bar{D}(1)$ ∞ Replacing $(\bar{D} + D)$ with 1 and replacing $(\bar{C} + C)$ with 1 (Use of Complement Law) $= \bar{A}\bar{B} + \bar{A}\bar{C}\bar{D}$ ∞ Reducing first four terms to $\bar{A}\bar{B}$ and reducing last two terms to $\bar{A}\bar{C}\bar{D}$ (Use of Identity Law) 1 mark for correct answer $= \bar{A}(\bar{B} + \bar{C}\bar{D})$	5																									

Answer 6

3(a)(i)	<div>AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr></table> <div>C</div>		00	01	11	10	0	1	1	0	1	1	1	1	0	1	1										
	00	01	11	10																							
0	1	1	0	1																							
1	1	1	0	1																							
3(a)(ii)	<div>1 mark for each correct loop</div> <div>AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr></table> <div>C</div>		00	01	11	10	0	1	1	0	1	1	1	1	0	1	2										
	00	01	11	10																							
0	1	1	0	1																							
1	1	1	0	1																							
3(a)(iii)	<div>1 mark per bullet point</div> <div><div>10</div><div>\overline{A}</div></div> <div><div>10</div><div>$+ \overline{B}$</div></div> <div>$X = \overline{A} + \overline{B}$</div>	2																									
3(b)(i)	<div>1 mark correct values and order of row and column headings</div> <div>3 marks fully correct table entries (based on headings) or 2 marks table entries contain one error (based on headings) or 1 mark table entries contain two errors (based on headings)</div> <div>AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>11</td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>10</td><td>1</td><td>1</td><td>0</td><td>0</td></tr></table> <div>CD</div>		00	01	11	10	00	0	0	1	1	01	0	0	1	1	11	1	1	0	0	10	1	1	0	0	4
	00	01	11	10																							
00	0	0	1	1																							
01	0	0	1	1																							
11	1	1	0	0																							
10	1	1	0	0																							
3(b)(ii)	<div>1 mark per loop</div> <div>AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>11</td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>10</td><td>1</td><td>1</td><td>0</td><td>0</td></tr></table> <div>CD</div>		00	01	11	10	00	0	0	1	1	01	0	0	1	1	11	1	1	0	0	10	1	1	0	0	2
	00	01	11	10																							
00	0	0	1	1																							
01	0	0	1	1																							
11	1	1	0	0																							
10	1	1	0	0																							
3(b)(iii)	<div>1 mark for each bullet point</div> <div><div>10</div><div>$\overline{A}.C$</div></div> <div><div>10</div><div>$+ A.\overline{C}$</div></div> <div>$X = \overline{A}.C + A.\overline{C}$</div>	2																									

Answer 7

4(a)	<p>1 mark for 3 or 4 correct products 2 marks for all 5 correct products</p> <p>$X = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C + A.B.C$</p>	2															
4(b)	<p>1 mark for correct answer</p> <p style="text-align: center;">AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr></table> <p style="text-align: center;">C</p>		00	01	11	10	0	1	0	0	0	1	1	1	1	1	1
	00	01	11	10													
0	1	0	0	0													
1	1	1	1	1													
4(c)	<p>1 mark per correct loop</p> <p style="text-align: center;">AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr></table> <p style="text-align: center;">C</p>		00	01	11	10	0	1	0	0	0	1	1	1	1	1	2
	00	01	11	10													
0	1	0	0	0													
1	1	1	1	1													
4(d)	<p>1 mark per bullet point.</p> <ul style="list-style-type: none">$\bar{A}\bar{B}$$+C$ <p>$X = \bar{A}\bar{B} + C \text{ // } X = C + \bar{A}\bar{B}$</p>	2															

Answer 8

2(a)(i)	1 mark for each 2 correct products, i.e. 3 marks for 6, 2 marks for 4 or 5, 1 mark for 2 or 3 $X = \overline{A}.\overline{B}.\overline{C} + \overline{A}.\overline{B}.C + \overline{A}.B.\overline{C} + \overline{A}.B.C + A.\overline{B}.\overline{C} + A.\overline{B}.C$	3																				
2(a)(ii)	1 mark for the correct K-map <div style="text-align: center;">AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>C</td><td></td><td></td><td></td><td></td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr></table>		00	01	11	10	C					0	1	1	0	1	1	1	1	0	1	1
	00	01	11	10																		
C																						
0	1	1	0	1																		
1	1	1	0	1																		
2(a)(iii)	1 mark for each correct loop <div style="text-align: center;">AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>C</td><td></td><td></td><td></td><td></td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr></table>		00	01	11	10	C					0	1	1	0	1	1	1	1	0	1	2
	00	01	11	10																		
C																						
0	1	1	0	1																		
1	1	1	0	1																		

2(a)(iv)	<p>1 mark per bullet point:</p> <ul style="list-style-type: none"> • \bar{A} • $+ \bar{B}$ <p>$X = \bar{A} + \bar{B} // X = \bar{B} + \bar{A}$</p>	2
2(b)	<p>$X = \overline{(\bar{W} + X) \cdot (Y + \bar{Z})}$</p> <p>One mark for correct use of <u>De Morgan's law</u> to +</p> <ul style="list-style-type: none"> • $X = \overline{(\bar{W} + X)} + \overline{(Y + \bar{Z})}$ <p>One mark for correct use of <u>De Morgan's law</u> + to</p> <ul style="list-style-type: none"> • $X = \bar{\bar{W}} \cdot \bar{X} + \bar{Y} \cdot \bar{\bar{Z}}$ <p>One mark for correct answer</p> <ul style="list-style-type: none"> • $X = W \cdot \bar{X} + \bar{Y} \cdot Z$ 	3

Answer 9

4(a)(i)	2 marks all products correct, 1 mark 2 or 3 products correct $X = \bar{A}.B.\bar{C} + \bar{A}.B.C + A.\bar{B}.\bar{C} + A.\bar{B}.C$	2																				
4(a)(ii)	1 mark for all correct bits <div style="text-align: center;">AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>C</td><td></td><td></td><td></td><td></td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td></tr></table>		00	01	11	10	C					0	0	1	0	1	1	0	1	0	1	1
	00	01	11	10																		
C																						
0	0	1	0	1																		
1	0	1	0	1																		
4(a)(iii)	1 mark for each correct loop <div style="text-align: center;">AB</div> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>C</td><td></td><td></td><td></td><td></td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td></tr></table>		00	01	11	10	C					0	0	1	0	1	1	0	1	0	1	2
	00	01	11	10																		
C																						
0	0	1	0	1																		
1	0	1	0	1																		
4(a)(iv)	1 mark per bullet – allow follow through from 4(a)(iii) $\infty \quad \bar{A}.B$ $\infty \quad +A.\bar{B}$ $X = \bar{A}.B + A.\bar{B}$	2																				

4(b)(i)	<p>1 mark per bullet max 2</p> <ul style="list-style-type: none">∞ Correct column headings and row headings – values only∞ Correct column headings and row headings – order <p>1 mark for 2 correct rows/columns, 2 marks for 4 correct rows/columns (based on headings) max 2</p> <div><div>AB</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>11</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>10</td><td>0</td><td>1</td><td>0</td><td>0</td></tr></table></div>		00	01	11	10	00	0	1	1	0	01	0	1	1	0	11	0	1	0	0	10	0	1	0	0	4
	00	01	11	10																							
00	0	1	1	0																							
01	0	1	1	0																							
11	0	1	0	0																							
10	0	1	0	0																							
4(b)(ii)	<p>1 mark for each correct loop</p> <div><div>CD</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>11</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>10</td><td>0</td><td>1</td><td>0</td><td>0</td></tr></table></div>		00	01	11	10	00	0	1	1	0	01	0	1	1	0	11	0	1	0	0	10	0	1	0	0	2
	00	01	11	10																							
00	0	1	1	0																							
01	0	1	1	0																							
11	0	1	0	0																							
10	0	1	0	0																							
4(b)(iii)	<p>1 mark per bullet</p> <p>$\bar{A}B$ $+B\bar{C}$ $X = \bar{A}B + B\bar{C}$</p>	2																									

Answer 10

4(a)(i)	1 mark for 2 or 3 correct, 2 marks for 4 correct $X = \bar{A}.B.\bar{C} + A.\bar{B}.\bar{C} + A.B.\bar{C} + A.B.C$	2															
4(a)(ii)	1 mark for the correct K-map <div><div>AB</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr></table><div>C</div></div>		00	01	11	10	0	0	0	1	0	1	0	1	1	1	1
	00	01	11	10													
0	0	0	1	0													
1	0	1	1	1													
4(a)(iii)	1 mark for each loop max 3 <div><div>AB</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr></table><div>C</div></div>		00	01	11	10	0	0	0	1	0	1	0	1	1	1	3
	00	01	11	10													
0	0	0	1	0													
1	0	1	1	1													

4(a)(iv)	<p>1 mark for each pair. Allow follow through from (iii)</p> <p>∴ A.B ∴ +B.C ∴ +A.C</p> <p>$X = A.B + B.C + A.C$</p>	3																									
4(b)(i)	<p>1 mark per bullet point max 2:</p> <p>∴ Correct column headings and row headings – values only ∴ Correct column headings and row headings – order</p> <p>1 mark for 2 correct rows or columns, 2 marks for 4 correct rows or columns (based on headings)</p> <div><div>AB</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>11</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>10</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table><div>CD</div></div>		00	01	11	10	00	0	1	1	0	01	0	0	1	0	11	0	0	1	0	10	0	0	1	0	4
	00	01	11	10																							
00	0	1	1	0																							
01	0	0	1	0																							
11	0	0	1	0																							
10	0	0	1	0																							
4(b)(ii)	<p>1 mark per loop</p> <div><div>AB</div><table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>11</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>10</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table><div>CD</div></div>		00	01	11	10	00	0	1	1	0	01	0	0	1	0	11	0	0	1	0	10	0	0	1	0	2
	00	01	11	10																							
00	0	1	1	0																							
01	0	0	1	0																							
11	0	0	1	0																							
10	0	0	1	0																							
4(b)(iii)	<p>1 mark per bullet point:</p> <p>∴ A.B ∴ +B.C̄.D̄</p> <p>$X = A.B + B.C̄.D̄$</p>	2																									

Answer 11

3(a)	<p>1 mark per bullet point to max 3:</p> <ul style="list-style-type: none"> Correct use of Idempotent law $Y = Y.Y$ $Y = Y + Y$ Correct use of Complement law $0 = Y.\bar{Y}$ $1 = Y + \bar{Y}$ Correct use of Distributive law $X(Y + Z) = X.Y + X.Z$ Correct use of Redundancy law $X\bar{Y} + Y = X + Y$ Correct use of identity law $X.1 = X$ <p>1 mark for the correct answer</p> <p>For example:</p> <div style="display: flex; justify-content: space-between; margin-top: 10px;"> <div style="width: 40%;"> $X = A.\bar{B}.\bar{C} + A.B.\bar{C} + A.B.C$ $X = A.\bar{B}.\bar{C} + A.B.\bar{C} + A.B.\bar{C} + A.B.C$ $X = A.\bar{C}.(B + B) + A.B.(C + C)$ $X = A.\bar{C} + A.B$ $X = A.(C + B)$ </div> <div style="width: 55%;"> <p>Idempotent law</p> <p>Distributive law</p> <p>Complement/Inverse law</p> <p>Correct answer</p> </div> </div> <div style="display: flex; justify-content: space-between; margin-top: 10px;"> <div style="width: 40%;"> $X = A.\bar{B}.\bar{C} + A.B.\bar{C} + A.B.C$ $X = A.\bar{C}.(B + B) + A.B.C$ $X = A.\bar{C} + A.B.C$ $X = A.(C + B.C)$ $X = A.(C + B)$ </div> <div style="width: 55%;"> <p>Distributive law</p> <p>Complement/Inverse law</p> <p>Redundancy Law</p> <p>Correct answer</p> </div> </div>																																				
3(b)(i)	<p>1 mark for first four as 0, 1 mark for 1011</p> <table style="margin-left: auto; margin-right: auto; border-collapse: collapse;"> <tr> <th style="padding: 5px;">A</th> <th style="padding: 5px;">B</th> <th style="padding: 5px;">C</th> <th style="padding: 5px;">X</th> </tr> <tr><td style="text-align: center;">0</td><td style="text-align: center;">0</td><td style="text-align: center;">0</td><td style="text-align: center;">0</td></tr> <tr><td style="text-align: center;">0</td><td style="text-align: center;">0</td><td style="text-align: center;">1</td><td style="text-align: center;">0</td></tr> <tr><td style="text-align: center;">0</td><td style="text-align: center;">1</td><td style="text-align: center;">0</td><td style="text-align: center;">0</td></tr> <tr><td style="text-align: center;">0</td><td style="text-align: center;">1</td><td style="text-align: center;">1</td><td style="text-align: center;">0</td></tr> <tr><td style="text-align: center;">1</td><td style="text-align: center;">0</td><td style="text-align: center;">0</td><td style="text-align: center;">1</td></tr> <tr><td style="text-align: center;">1</td><td style="text-align: center;">0</td><td style="text-align: center;">1</td><td style="text-align: center;">0</td></tr> <tr><td style="text-align: center;">1</td><td style="text-align: center;">1</td><td style="text-align: center;">0</td><td style="text-align: center;">1</td></tr> <tr><td style="text-align: center;">1</td><td style="text-align: center;">1</td><td style="text-align: center;">1</td><td style="text-align: center;">1</td></tr> </table> <div style="display: flex; justify-content: center; align-items: center; margin-top: 10px;"> <div style="text-align: center;"> <div style="font-size: 4em; margin: 0 10px;">}</div> <div>1 mark</div> </div> <div style="text-align: center; margin-top: 20px;"> <div style="font-size: 4em; margin: 0 10px;">}</div> <div>1 mark</div> </div> </div>	A	B	C	X	0	0	0	0	0	0	1	0	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	0	1	1	0	1	1	1	1	1
A	B	C	X																																		
0	0	0	0																																		
0	0	1	0																																		
0	1	0	0																																		
0	1	1	0																																		
1	0	0	1																																		
1	0	1	0																																		
1	1	0	1																																		
1	1	1	1																																		
3(b)(ii)	<p>1 mark for correct K-map</p> <div style="text-align: center; margin: 10px 0;"> AB </div> <table style="margin-left: auto; margin-right: auto; border-collapse: collapse;"> <tr> <td></td> <td></td> <td style="padding: 5px;">00</td> <td style="padding: 5px;">01</td> <td style="padding: 5px;">11</td> <td style="padding: 5px;">10</td> </tr> <tr> <td rowspan="2" style="vertical-align: middle; padding: 5px;">C</td> <td style="padding: 5px;">0</td> <td style="text-align: center; padding: 5px;">0</td> <td style="text-align: center; padding: 5px;">0</td> <td style="text-align: center; padding: 5px;">1</td> <td style="text-align: center; padding: 5px;">1</td> </tr> <tr> <td style="padding: 5px;">1</td> <td style="text-align: center; padding: 5px;">0</td> <td style="text-align: center; padding: 5px;">0</td> <td style="text-align: center; padding: 5px;">1</td> <td style="text-align: center; padding: 5px;">0</td> </tr> </table>			00	01	11	10	C	0	0	0	1	1	1	0	0	1	0																			
		00	01	11	10																																
C	0	0	0	1	1																																
	1	0	0	1	0																																

3(b)(iii)	<p>1 mark for each correct loop to max 2</p> <p style="text-align: center;">AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table>		00	01	11	10	0	0	0	1	1	1	0	0	1	0										
	00	01	11	10																						
0	0	0	1	1																						
1	0	0	1	0																						
3(b)(iv)	<p>1 mark per bullet point:</p> <ul style="list-style-type: none">• $A\bar{C}$• $+ A.B$ <p>$X = A\bar{C} + A.B$</p>																									
3(c)(i)	<p>1 mark per bullet point to max 2:</p> <ul style="list-style-type: none">• Correct column headings and row headings – values only• Correct column headings and row headings – order <p>1 mark for 2 correct rows or columns, 2 marks for 4 correct rows or columns (based on headings)</p> <p style="text-align: center;">AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>11</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>10</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table>		00	01	11	10	00	0	1	1	0	01	0	0	1	0	11	0	0	1	0	10	0	0	1	0
	00	01	11	10																						
00	0	1	1	0																						
01	0	0	1	0																						
11	0	0	1	0																						
10	0	0	1	0																						
3(c)(ii)	<p>1 mark for each correct loop to max 2:</p> <p style="text-align: center;">AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>11</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>10</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table>		00	01	11	10	00	0	1	1	0	01	0	0	1	0	11	0	0	1	0	10	0	0	1	0
	00	01	11	10																						
00	0	1	1	0																						
01	0	0	1	0																						
11	0	0	1	0																						
10	0	0	1	0																						
3(c)(iii)	<p>1 mark per bullet point:</p> <ul style="list-style-type: none">• $A.B$• $+ B.\bar{C}.\bar{D}$ <p>$X = A.B + B.\bar{C}.\bar{D}$</p>																									

Answer 12

3(a)	$X = A.(\bar{B} + (B . C))$ $B.C$ $\bar{B} + B.C$ $A.$	1 1 1	3
------	---	-------------	----------

3(b)	<table><tr><th>A</th><th>B</th><th>C</th><th>Working Space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table> <p>1 mark first four entries, 1 mark for the last four entries</p>	A	B	C	Working Space	X	0	0	0		0	0	0	1		0	0	1	0		0	0	1	1		0	1	0	0		1	1	0	1		1	1	1	0		0	1	1	1		1	2
A	B	C	Working Space	X																																											
0	0	0		0																																											
0	0	1		0																																											
0	1	0		0																																											
0	1	1		0																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		0																																											
1	1	1		1																																											
3(c)(i)	<p style="text-align: center;">AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>C 0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td></tr></table>		00	01	11	10	C 0	0	0	0	1	1	0	0	1	1	1																														
	00	01	11	10																																											
C 0	0	0	0	1																																											
1	0	0	1	1																																											
3(c)(ii)	<p style="text-align: center;">AB</p> <table><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>C 0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td></tr></table>		00	01	11	10	C 0	0	0	0	1	1	0	0	1	1	2																														
	00	01	11	10																																											
C 0	0	0	0	1																																											
1	0	0	1	1																																											
3(c)(iii)	$X = A.\bar{B} + A.C$ <div>1 1</div>	2																																													
3(d)	$X = A.(\bar{B} + (B.C))$ $X = A.(\bar{B} + C)$ $X = A.\bar{B} + A.C$ <div>1 1 (dependent mark – must be correct outcome from previous line)</div>	2																																													

Answer 13

3(a)	$S = (\bar{P} + (\overline{Q+R})) . R$ <div style="display: flex; justify-content: space-between;"> <div> \bar{P} $(\overline{Q+R})$ $(\bar{P} + (\overline{Q+R}))$ $. R$ (must be outside final brackets) </div> <div> 1 1 1 1 </div> </div> <p>Or</p> <div style="display: flex; justify-content: space-between;"> <div> \bar{P} $(\overline{Q+R})$ $\bar{P} + (\overline{Q+R})$ $(.....) . R$ </div> <div> 1 1 1 1 </div> </div>	4
------	---	---

3(b)	<table><tr><th>P</th><th>Q</th><th>R</th><th>Working space</th><th>S</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table> <p>2 marks all correct, 1 mark seven correct, 0 marks six or fewer correct</p>	P	Q	R	Working space	S	0	0	0		0	0	0	1		1	0	1	0		0	0	1	1		1	1	0	0		0	1	0	1		0	1	1	0		0	1	1	1		0	2
P	Q	R	Working space	S																																											
0	0	0		0																																											
0	0	1		1																																											
0	1	0		0																																											
0	1	1		1																																											
1	0	0		0																																											
1	0	1		0																																											
1	1	0		0																																											
1	1	1		0																																											
3(c)(i)	<table><tr><td></td><td colspan="4">PQ</td></tr><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>R</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td></td><td>1</td><td>1</td><td>1</td><td>0</td></tr><tr><td></td><td></td><td></td><td>0</td><td>0</td></tr></table>		PQ					00	01	11	10	R	0	0	0	0		1	1	1	0				0	0	1																				
	PQ																																														
	00	01	11	10																																											
R	0	0	0	0																																											
	1	1	1	0																																											
			0	0																																											
3(c)(ii)	<table><tr><td></td><td colspan="4">PQ</td></tr><tr><td></td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>R</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td></td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td></td><td></td><td></td><td>0</td><td>0</td></tr></table>		PQ					00	01	11	10	R	0	0	0	0		1	1	0	0				0	0	1																				
	PQ																																														
	00	01	11	10																																											
R	0	0	0	0																																											
	1	1	0	0																																											
			0	0																																											
3(c)(iii)	$S = \bar{P} \cdot R$	1																																													
3(d)	$S = (\bar{P} + (\bar{Q} + R)) \cdot R$ $S = (\bar{P} + (\bar{Q} \cdot \bar{R})) \cdot R \quad // \quad \bar{P} \cdot R + (\bar{Q} + R) \cdot R$ $S = (\bar{P} \cdot R) + (\bar{Q} \cdot \bar{R} \cdot R)$ $S = \bar{P} \cdot R + \bar{Q} \cdot 0$ $S = \bar{P} \cdot R + 0$ $S = \bar{P} \cdot R$	3																																													

Answer 14

5(a)(i)	<table> <tr> <th>A</th><th>B</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	1
A	B	X															
0	0	1															
0	1	1															
1	0	1															
1	1	0															

5(a)(ii)	<table><tr><th>A</th><th>B</th><th>C</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	X	0	0	0	1	0	0	1	1	0	1	0	1	0	1	1	1	1	0	0	1	1	0	1	1	1	1	0	1	1	1	1	0	1																																								
A	B	C	X																																																																											
0	0	0	1																																																																											
0	0	1	1																																																																											
0	1	0	1																																																																											
0	1	1	1																																																																											
1	0	0	1																																																																											
1	0	1	1																																																																											
1	1	0	1																																																																											
1	1	1	0																																																																											
5(b)(i)	<table><tr><td></td><td>S</td><td>R</td><td>Q</td><td>\bar{Q}</td><td></td></tr><tr><td>Initially</td><td>1</td><td>0</td><td>0</td><td>1</td><td></td></tr><tr><td>R changed to 1</td><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>S changed to 0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>S changed to 1</td><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>S and R changed to 0</td><td>0</td><td>0</td><td>1</td><td>1</td><td></td></tr></table>		S	R	Q	\bar{Q}		Initially	1	0	0	1		R changed to 1	1	1	0	1	1	S changed to 0	0	1	1	0	1	S changed to 1	1	1	1	0	1	S and R changed to 0	0	0	1	1		3																																								
	S	R	Q	\bar{Q}																																																																										
Initially	1	0	0	1																																																																										
R changed to 1	1	1	0	1	1																																																																									
S changed to 0	0	1	1	0	1																																																																									
S changed to 1	1	1	1	0	1																																																																									
S and R changed to 0	0	0	1	1																																																																										
5(b)(ii)	<ul style="list-style-type: none">Q and \bar{Q} have same valueQ and \bar{Q} should be complements of each otherFlip-flop becomes unstable <p>1 mark for each point, max 2</p>	2																																																																												
5(c)(i)	<table><tr><th rowspan="2">J</th><th rowspan="2">K</th><th rowspan="2">Clock</th><th rowspan="2">Working space</th><th colspan="2">Initial values</th><th colspan="2">Final values</th></tr><tr><th>Q</th><th>\bar{Q}</th><th>Q</th><th>\bar{Q}</th></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td><td>1</td><td>1</td><td>0</td></tr></table> <p>1 mark per shaded row</p>	J	K	Clock	Working space	Initial values		Final values		Q	\bar{Q}	Q	\bar{Q}	0	0	1		1	0	1	0	0	0	1		0	1	0	1	0	1	1		1	0	0	1	0	1	1		0	1	0	1	1	0	1		1	0	1	0	1	0	1		0	1	1	0	1	1	1		1	0	0	1	1	1	1		0	1	1	0	4
J	K					Clock	Working space	Initial values		Final values																																																																				
		Q	\bar{Q}	Q	\bar{Q}																																																																									
0	0	1		1	0	1	0																																																																							
0	0	1		0	1	0	1																																																																							
0	1	1		1	0	0	1																																																																							
0	1	1		0	1	0	1																																																																							
1	0	1		1	0	1	0																																																																							
1	0	1		0	1	1	0																																																																							
1	1	1		1	0	0	1																																																																							
1	1	1		0	1	1	0																																																																							
5(c)(ii)	<ul style="list-style-type: none">S-R flip-flop has an invalid combination of S and R // The S_R flip flop allows both Q and \bar{Q} to have the same value // S-R flip-flop inputs may arrive at different times 1The J-K flip-flop does not allow for Q and \bar{Q} to have the same value // All four combination of values for J and K are valid // J-K flip-flop incorporates a clock pulse for synchronisation 1	2																																																																												
5(d)	<ul style="list-style-type: none">A flip-flop can store either a 0 or a 1Computers use bits to store dataFlip-flops can therefore be used to store bits (of data)Memory can be created from flip-flops <p>1 mark for valid point, max 2</p>	2																																																																												

Answer 15

5(a)	<table><tr><td>A</td><td>B</td><td>X</td></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0	1																					
A	B	X																																				
0	0	1																																				
0	1	0																																				
1	0	0																																				
1	1	0																																				
5(b)	<table><tr><td></td><td>S</td><td>R</td><td>Q</td><td>\bar{Q}</td><td></td></tr><tr><td>Initially</td><td>1</td><td>0</td><td>1</td><td>0</td><td></td></tr><tr><td>S changed to 0</td><td>0</td><td>0</td><td>1</td><td>0</td><td>(1)</td></tr><tr><td>R changed to 1</td><td>0</td><td>1</td><td>0</td><td>1</td><td>(1)</td></tr><tr><td>R changed to 0</td><td>0</td><td>0</td><td>0</td><td>1</td><td>(1)</td></tr><tr><td>S and R changed to 1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>(1)</td></tr></table>		S	R	Q	\bar{Q}		Initially	1	0	1	0		S changed to 0	0	0	1	0	(1)	R changed to 1	0	1	0	1	(1)	R changed to 0	0	0	0	1	(1)	S and R changed to 1	1	1	0	0	(1)	4
	S	R	Q	\bar{Q}																																		
Initially	1	0	1	0																																		
S changed to 0	0	0	1	0	(1)																																	
R changed to 1	0	1	0	1	(1)																																	
R changed to 0	0	0	0	1	(1)																																	
S and R changed to 1	1	1	0	0	(1)																																	
5(c)(i)	Clock (pulse)	1																																				
5(c)(ii)	<p>Max 2 marks per problem – max 4 marks</p> <p>Problem 1</p> <ul style="list-style-type: none">One combination of S and R gives NOT valid / indeterminate output // Q and \bar{Q} have the same valueThe JK flip-flop does not allow for Q and \bar{Q} to have the same value for any combination of inputs // \bar{Q} and Q have to be complementary <p>Problem 2</p> <ul style="list-style-type: none">Inputs may not arrive at the same timeThe JK flip-flop has a clock pulse to synchronise inputs	4																																				

Answer 16

5 (a)																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
-------	--	--	--	--	--

(ii)	$S = 0 \ R = 0$ Produces $\underline{Q} = 1$, $\overline{Q} = 1$ // Q and \overline{Q} have same value But Q and \overline{Q} should be complements of each other Becomes unstable	1 1 1 1 Max 3
(c) (i)	Clock (pulse)	1
(ii)	All four possibilities are valid The 1-1 combination changes output to logical complement Unstable state avoided Invalid state cannot occur // the flip-flop is stable	1 1 1 1 Max 1
(d)	Memory // data storage Stores a single bit	1 1

Answer 17

4 (a) (i)

Input		Output	
X	Y	A	B
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

1 mark for each
correct column
(A and B)

[2]

(ii) Half adder

[1]

(iii) C // Carry
S // Sum

[1]

[1]

represents the carry part of the addition of two bits

[1]

represents the sum part of the addition of two bits

[1]

(b) (i) A.

[1]

(A.B + C)

[1]

(ii) Allow follow through from (b)(i)

$$\begin{aligned}
 &A.(A.B+C) \\
 &= A.A.B + A.C \\
 &= A.B + A.C \\
 &= A.(B+C)
 \end{aligned}$$

1 mark for each correct simplification line – max 2

[2]

1 mark for A.(B+C) if correct answer to part (b)(i)

[1]

Answer 18

5 (a) (i)

Input			Working space	Output	
P	Q	R		J	K
0	0	0		0	0
0	0	1		0	1
0	1	0		0	1
0	1	1		1	0
1	0	0		0	1
1	0	1		1	0
1	1	0		1	0
1	1	1		1	1

1 mark each column

If zero marks then
6 or 7 pairs correct – 1 mark

[2]

(ii) Full adder

[1]

(iii) C / Carry

[1]

S / Sum

[1]

represents the carry part of the addition of three bits

[1]

represents the sum part of the addition of three bits

[1]

(b) (i) A.

[1]

$(A+B).C$

[1]

(ii) Allow follow through from (b)(i)

$$\begin{aligned}
 &A. ((A+B).C) \\
 &= A.(A.C + B.C) \\
 &= A.A.C + A.B.C \\
 &= A.C + A.B.C \\
 &= A.C (1 + B) \\
 &= A.C.1 \\
 &= A.C
 \end{aligned}$$

1 mark for each correct simplification line – max 3 [3]

1 mark for A.C if correct answer to part (b)(i) [1]

[4]

Answer 19

4 (a) (i)	Circuit 1			1
	A	B	X	
	0	0	1	
	0	1	1	
	1	0	1	
	1	1	0	

(ii)	<table><tr><th colspan="3">Circuit 2</th></tr><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	Circuit 2			A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	1
Circuit 2																				
A	B	X																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		
(b) (i)	<ul style="list-style-type: none">circuit 1: $\overline{A.B}$circuit 2: $\overline{A + B}$	1 1																		
(ii)	$\overline{A.B} \equiv \overline{A + B}$	1																		
(c)	$\overline{\overline{(A + B).B}}$ Mark as follows: $\overline{(A + B)}$ $\overline{.B}$ bar over whole expression	1 1 1																		
(d)	$\overline{\overline{(A + B).B}}$ $= \overline{(A + B) + \overline{B}}$ $= (A + B) + \overline{\overline{B}}$ $= A + (B + \overline{B})$ $= A + 1$ $= 1$ allow f.t. from (c)	1 1 1 1 1 [max 3]																		

Question 20

5 (a) (i) $\overline{A}.B.C + A.B.\overline{C} + A.B.C$ [1]
[1]
[1]

(ii)

		AB			
		00	01	11	10
C	0	0	0	1	0
	1	0	1	1	0

[1]

(iii)

		AB			
		00	01	11	10
C	0	0	0	1	0
	1	1	0	1	0

1 mark for each loop

Allow f.t. from (ii)

[2]

(iv) $X =$

$$A.B + B.C$$

Allow f.t. from (iii)

[1]

[1]

(b) (i)

		AB			
		00	01	11	10
CD	00	0	1	1	0
	01	0	0	0	0
	11	0	0	1	0
	10	0	1	1	0

1 mark row headings

1 mark column headings

1 mark per 2 correct rows (based on headings)

[4]

(ii)

		AB			
		00	01	11	10
CD	00	0	1	1	0
	01	0	0	0	0
	11	0	0	1	0
	10	0	1	1	0

1 mark for loop with two 1s

1 mark for looping the four 1s

[2]

(iii) $X =$

$$B.\bar{D} + A.B.C$$

[1]

[1]

Answer 21

5 (a) (i)

$$Z = P \cdot \overline{Q} \cdot \overline{R} + P \cdot \overline{Q} \cdot R + P \cdot Q \cdot R$$

[1]
[1]
[1]

(ii)

		PQ			
		00	01	11	10
R	0	0	0	0	1
	1	0	0	1	1

[1]

(iii) 1 mark each loop

		PQ			
		00	01	11	10
R	0	0	0	0	1
	1	0	0	1	1

Allow f.t. from (ii)

[2]

(iv)

$$Z = P \cdot \overline{Q} + P \cdot R$$

[1]
[1]

Allow f.t. from (iii)

(b) (i) 1 mark row headings. 1 mark column headings.
1 mark per 2 correct rows (based on headings)

		PQ			
		00	01	11	10
RS	00	0	0	0	0
	01	0	1	1	1
	11	0	1	1	0
	10	0	0	0	0

[4]

- (ii) 1 mark for loop with two 1s; 1 mark for loop with four 1s

		PQ			
		00	01	11	10
RS	00	0	0	0	0
	01	0	1	1	1
	11	0	1	1	0
	10	0	0	0	0

Allow f.t. from (i)

–1 for each incorrect grouping, max. 2 errors

[2]

- (iii)

Z =

Q.S

[1]

+P.R. \bar{S}

[1]

Allow f.t. from (ii), –1 error if more than 2 terms

[Total: 16]