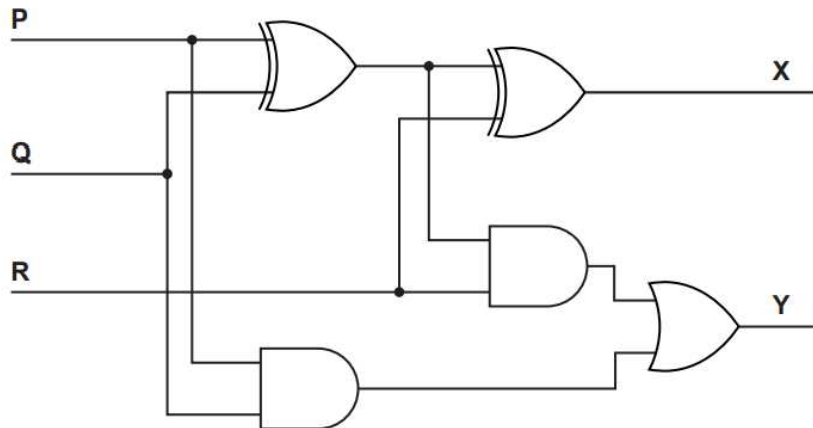


# Logic Gates

## Question 1

- 4 (a) Write the Boolean algebraic expressions for the following logic circuit.



X = .....

Y = .....

[5]

- (b) The logic circuit given in **part (a)** is a full adder.

- (i) Give the purpose of outputs **X** and **Y** in this circuit.

X .....

Y .....

[2]

- (ii) Give the use of the input **R** in this circuit.

..... [1]

## Question 2

- 4 The following truth table represents a logic circuit with three inputs and two outputs.

INPUT			OUTPUT	
A	B	C	X	Y
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- (a) Write the Boolean expressions for the truth table as sum-of-products.

X = .....

.....

Y = .....

.....

[4]

- (b) Complete the Karnaugh Maps (K-maps) for the truth table.

		OUTPUT X						OUTPUT Y			
		AB						AB			
		00	01	11	10			00	01	11	10
C	0					C	0				
	1						1				

[2]

- (c) The K-maps can be used to simplify **one** of the expressions in **part (a)**.

- (i) Draw loop(s) around appropriate group(s) of 1s to produce an optimal sum-of-products for the single output table that can be simplified in **part (b)**. [3]

- (ii) Write the simplified sum-of-products expressions for this output from **part (c)(i)**.

..... [3]

- (d) Identify the common logic circuit given by the truth table in **part (a)**. Give the use of each output.

Logic circuit .....

Use of **X** .....

Use of **Y** .....

[3]

### Question 3

- 4 The following truth table represents a logic circuit with three inputs and two outputs.

INPUT			OUTPUT	
A	B	C	X	Y
0	0	0	1	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1

- (a) Write the Boolean expressions for the truth table as sum-of-products.

**X** = .....

**Y** = .....

[3]

- (b) Complete the Karnaugh Maps (K-maps) for the truth table.

		OUTPUT X						OUTPUT Y			
		AB						AB			
		00	01	11	10			00	01	11	10
C	0					C	0				
	1						1				

[2]

(c) The K-maps can be used to simplify **one** of the expressions in **part (a)**.

(i) Draw loop(s) around appropriate group(s) of 1s to produce an optimal sum-of-products for the single output table that can be simplified in **part (b)**. [2]

(ii) Write the simplified sum-of-products expressions for this output from **part (c)(i)**.

..... [2]

## Question 4

5 Complete these statements about flip-flops.

A flip-flop is a .....

It has ..... stable states.

A flip-flop is used for .....


There are different types of flip-flop, for example ..... and

.....

[5]
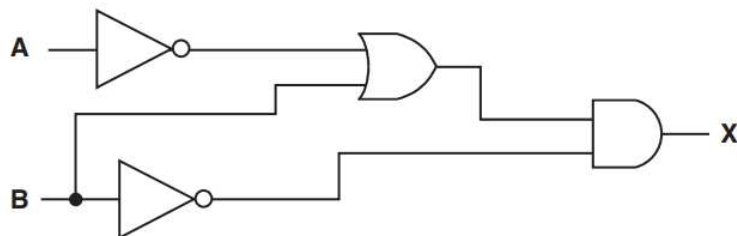
## Question 5


3 (a) The following logic circuit can be simplified to use only one gate.



Give the name of this single gate.

..... [1]

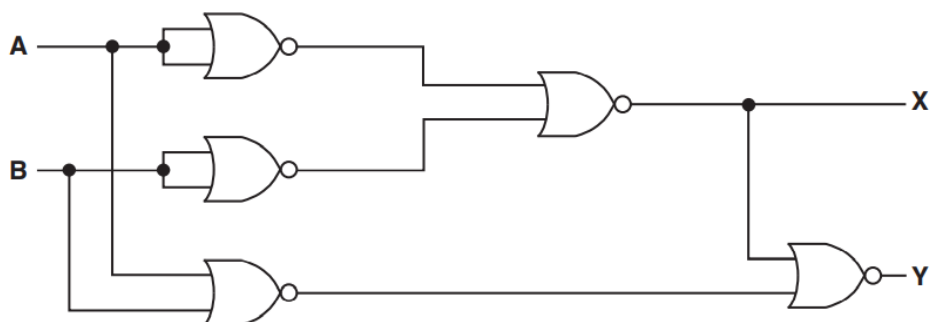(b) (i) Complete the truth table for the logic circuit.



A	B	Working space	X	Y
0	0			
0	1			
1	0			
1	1			

[2]

(ii) Give the name of the logic circuit that has this truth table.

..... [1]

(iii) Give the uses for outputs **X** and **Y**.

**X** .....

**Y** .....

[2]

(c) Consider the following Boolean algebraic expression:

$$\overline{A} . \overline{B} . \overline{C} . \overline{D} + \overline{A} . \overline{B} . \overline{C} . D + \overline{A} . \overline{B} . C . D + \overline{A} . \overline{B} . C . \overline{D} + \overline{A} . B . \overline{C} . \overline{D}$$

Use Boolean algebra to simplify the expression. Show your working.

Working .....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

Simplified expression ..... [5]

## Question 6

- 3 (a) A Boolean algebraic expression produces the following truth table.

INPUT			OUTPUT
A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- (i) Complete the Karnaugh Map (K-map) for the truth table.

		AB			
		00	01	11	10
C	0				
	1				

[1]

The K-map can be used to simplify the expression that produced the truth table in **part (a)**.

- (ii) Draw loops around appropriate groups of 1s in the K-map to produce an optimal sum-of-products. [2]

- (iii) Write the simplified sum-of-products Boolean expression for the truth table.

**X** = ..... [2]

(b) A logic circuit with four inputs produces the following truth table.

INPUT				OUTPUT
A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

(i) Complete the K-map for the truth table.

		AB			
CD					

[4]

(ii) Draw loops around appropriate groups of 1s in the K-map to produce an optimal sum-of-products. [2]

(iii) Write the simplified sum-of-products Boolean algebraic expression for the truth table.

**X** = ..... [2]

## Question 7

- 4 A Boolean expression produces the following truth table.

INPUT			OUTPUT
A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- (a) Write the Boolean expression for the truth table as a sum-of-products.

X = ..... [2]

- (b) Complete the Karnaugh Map (K-map) for the truth table above.

		AB			
		00	01	11	10
C	0				
	1				

[1]

The K-map can be used to simplify the expression in **part (a)**.

- (c) Draw loops around appropriate groups in the K-map in **part (b)** to produce an optimal sum-of-products. [2]

- (d) Write, using your answer to **part (c)**, a simplified sum-of-products expression for the truth table.

X = ..... [2]



## Question 8

- 2 (a) A Boolean expression produces the following truth table.

INPUT			OUTPUT
A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- (i) Write the Boolean expression for the truth table by applying the sum-of-products.

X = .....  
 ..... [3]

- (ii) Complete the Karnaugh Map (K-map) for the truth table in **part (a)**.

		AB			
		00	01	11	10
C	0				
	1				

[1]

The K-map can be used to simplify the function in **part (a)(i)**.

- (iii) Draw loop(s) around appropriate groups in the table in **part (a)(ii)**, to produce an optimal sum-of-products. [2]
- (iv) Write, using your answer to **part (a)(iii)**, a simplified Boolean expression for your Karnaugh map.

X = ..... [2]

- (b) Simplify the following expression using De Morgan's laws. Show your working.

$$\overline{(\overline{W + X}) \cdot (Y + \overline{Z})}$$

.....

.....

.....

.....

.....

..... [3]

## Question 9

- 4 (a) A Boolean expression produces the following truth table.

INPUT			OUTPUT
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- (i) Write the Boolean expression for the truth table as a sum-of-products.

X = ..... [2]

- (ii) Complete the Karnaugh Map (K-map) for the truth table in **part (a)(i)**.

		AB			
		00	01	11	10
C	0				
	1				

[1]

The K-map can be used to simplify the function in **part (a)(i)**.

- (iii) Draw loop(s) around appropriate group(s) of 1s to produce an optimal sum-of-products for the table in **part (a)(ii)**. [2]

- (iv) Write the simplified sum-of-products expression for your answer to **part (a)(iii)**.

X = ..... [2]

(b) A logic circuit with four inputs produces the following truth table.

INPUT				OUTPUT
A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

(i) Complete the K-map that corresponds to the truth table.

		AB			
CD					

[4]

(ii) Draw loop(s) around appropriate group(s) of 1s to produce an optimal sum-of-products for the table in **part (b)(i)**. [2]

(iii) Write the simplified sum-of-products expression for your answer to **part (b)(ii)**.

X = ..... [2]

## Question 10

- 4 (a) A Boolean expression corresponds to the following truth table.

INPUT			OUTPUT
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- (i) Write the Boolean expression for the truth table by applying the sum-of-products.

X = .....[2]

- (ii) Complete the Karnaugh Map (K-map) for the truth table.

		AB			
		00	01	11	10
C	0				
	1				

[1]

- (iii) The K-map can be used to simplify the expression in **part (a)(i)**.

Draw loop(s) around appropriate groups of 1s in the table in **part (a)(ii)** to produce an optimal sum-of-products. [3]

- (iv) Write the simplified sum-of-products expression for your answer to **part (a)(iii)**.

X = .....[3]

(b) A logic circuit with four inputs produces the following truth table.

INPUT				OUTPUT
A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

(i) Complete the K-map that corresponds to the truth table.

		AB			
CD					

[4]

(ii) Draw loop(s) around appropriate groups of 1s in the table in **part (b)(i)** to produce an optimal sum-of-products. [2]

(iii) Write the simplified sum-of-products expression for your answer to **part (b)(ii)**.

X = ..... [2]

### Question 11


- 3 (a)** Consider the following Boolean expression.

$$A \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot \bar{C} + A \cdot B \cdot C$$

Use Boolean algebra to simplify the expression.

.....[4]

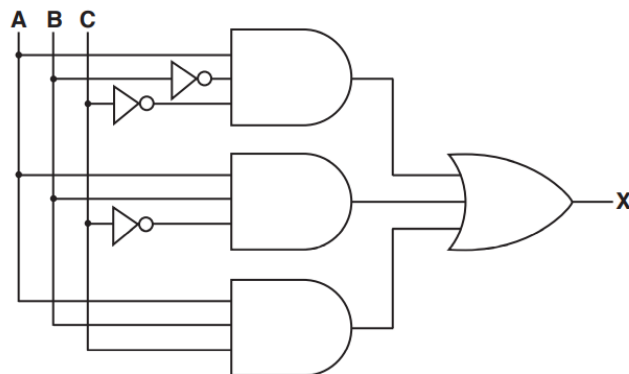- (b) (i)** Complete the truth table for the following logic circuit.



A	B	C	Working space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

- (ii) Complete the Karnaugh Map (K-map) for the truth table in **part (b)(i)**.

		AB			
		00	01	11	10
C	0				
	1				

[1]

- (iii) Draw loops around appropriate groups of 1s in the table in **part (b)(ii)** to produce an optimal sum-of-products. [2]

- (iv) Using your answer to **part (b)(iii)**, write a simplified sum-of-products Boolean expression.

**X** = .....[2]

- (c) The truth table for a logic circuit with four inputs is shown.

INPUT				OUTPUT
A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

- (i) Complete the K-map for the truth table in **part (c)**.

		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				

[4]


- (ii) Draw loops around appropriate groups of 1s in the table in **part (c)(i)** to produce an optimal sum-of-products. [2]

- (iii) Using your answer to **part (c)(ii)**, write a simplified sum-of-products Boolean expression.

X = ..... [2]
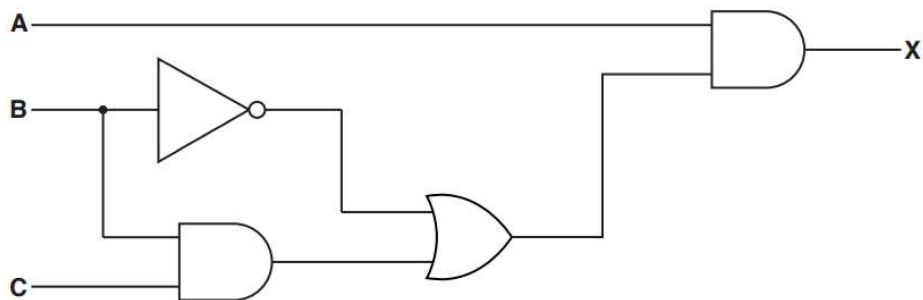
## Question 12

- 3 Consider the following logic circuit, which contains a redundant logic gate.



- (a) Write the Boolean algebraic expression corresponding to this logic circuit.

X = ..... [3]

- (b) Complete the truth table for this logic circuit.

A	B	C	Working space	X
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[2]



- (c) (i) Complete the Karnaugh Map (K-map) for the truth table in **part (b)**.

		AB			
		00	01	11	10
C	0				
	1				

The K-map can be used to simplify the expression in **part (a)**.

[1]

- (ii) Draw loop(s) around appropriate groups to produce an optimal sum-of-products. [2]

- (iii) Write a simplified sum-of-products expression, using your answer to **part (ii)**.

X = .....[2]

- (d) One Boolean identity is:


$$A + \bar{A}.B = A + B$$

Simplify the expression for X in **part (a)** to the expression for X in **part (c)(iii)**. You should use the given identity.

.....  
 .....  
 .....  
 .....[2]

## Question 13

- 3 A logic circuit is shown:

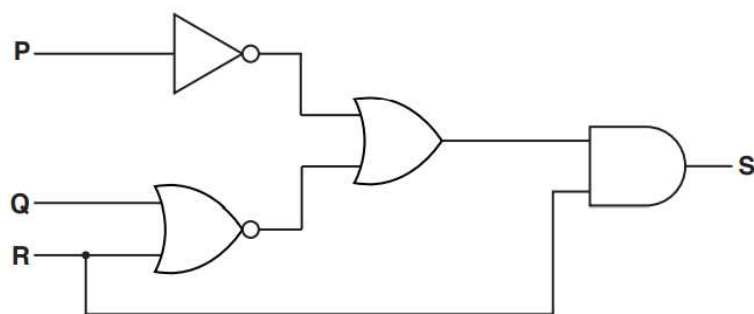

- (a) Write the Boolean algebraic expression corresponding to this logic circuit:

S = .....[4]

**(b)** Complete the truth table for this logic circuit:

P Q R			Working space	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[2]

(c) (i) Complete the Karnaugh Map (K-map) for the truth table in **part (b)**.

		PQ			
		00	01	11	10
R	0				
	1				

[1]

The K-map can be used to simplify the function in **part (a)**.

(ii) Draw loop(s) around appropriate groups to produce an optimal sum-of-products. [1]

(iii) Write a simplified sum-of-products expression, using your answer to **part (ii)**.

$S =$  .....[1]

(d) One Boolean identity is:

$$(A + B) \cdot C = A \cdot C + B \cdot C$$

Simplify the expression for S in **part (a)** to the expression for S in **part (c)(iii)**.


You should use the given identity and De Morgan's Laws.

.....[3]

[3]
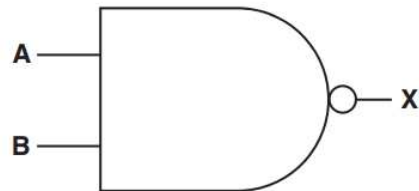
## Question 14


- 5 (a) (i) Complete the truth table for this 2-input NAND gate:



A	B	X
0	0	
0	1	
1	0	
1	1	

[1]

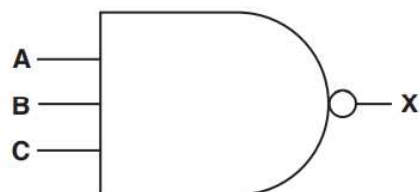
- (ii) Complete the truth table for this 3-input NAND gate:



A	B	C	X
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

[1]

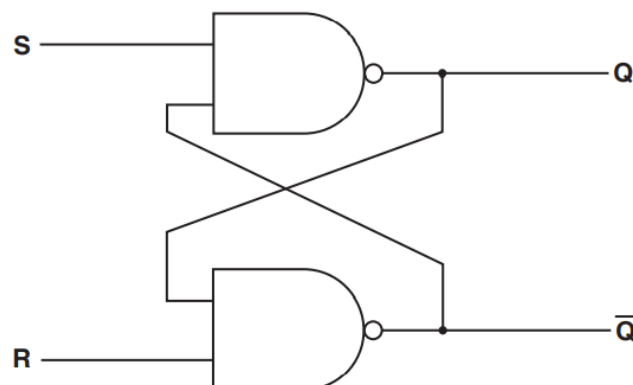- (b) A SR flip-flop is constructed using two NAND gates.



- (i) Complete the truth table for the SR flip-flop:

	S	R	Q	$\bar{Q}$
Initially	1	0	0	1
R changed to 1	1	1		
S changed to 0	0	1		
S changed to 1	1	1		
S and R changed to 0	0	0	1	1

[3]

- (ii) The final row in the table in **part b(i)** shows that the output for both **Q** and  $\overline{Q}$  is 1.

Explain why this is a problem.

.....


.....

.....

..... [2]

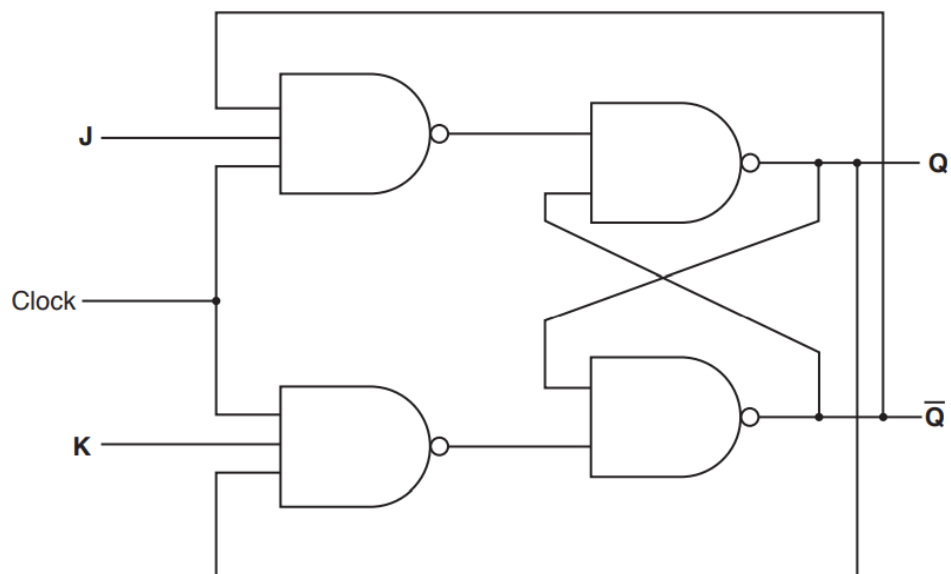- (c) Another type of flip-flop is the JK flip-flop.

A JK flip-flop is constructed as follows:



- (i) Complete this truth table for the JK flip-flop.

J	K	Clock	Working space	Initial values		Final values	
				Q	$\overline{Q}$	Q	$\overline{Q}$
0	0	1		1	0	1	0
0	0	1		0	1	0	1
0	1	1		1	0	0	1
0	1	1		0	1	0	1
1	0	1		1	0		
1	0	1		0	1		
1	1	1		1	0		
1	1	1		0	1		

[4]

(ii) Explain why the JK flip-flop is an improvement on the SR flip-flop.

.....

.....

..... [2]

(d) Explain the role of flip-flops in a computer.


.....

.....

..... [2]
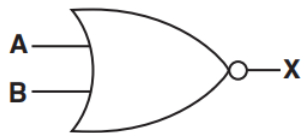
## Question 15


5 (a) Complete the truth table for this NOR gate:



A	B	X
0	0	
0	1	
1	0	
1	1	

[1]

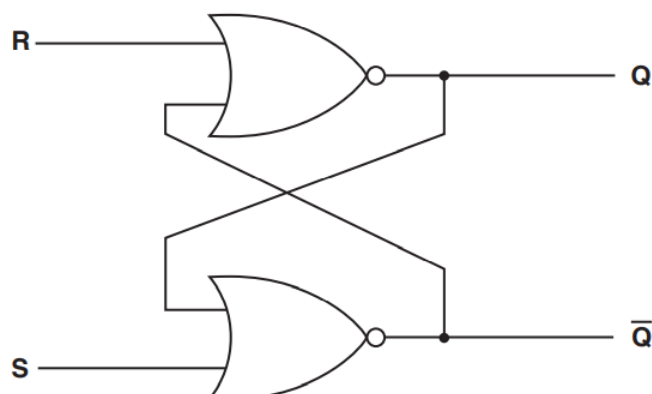A SR flip-flop is constructed using two NOR gates.



(b) Complete the truth table for the SR flip-flop:

	S	R	Q	$\bar{Q}$
Initially	1	0	1	0
S changed to 0	0	0		
R changed to 1	0	1		
R changed to 0	0	0		
S and R changed to 1	1	1		

[4]

Another type of flip-flop is the JK flip-flop. The JK flip-flop is an improvement on the SR flip-flop.

(c) (i) The JK flip-flop has three inputs. Two of the inputs are the Set (J) and the Reset (K).

State the third input.

.....[1]

(ii) There are **two** problems with the SR flip-flop that the JK flip-flop overcomes.

State each problem and state why it does not occur for the JK flip-flop.

Problem 1 .....

.....

.....

.....

Problem 2 .....

.....


.....

.....

[4]
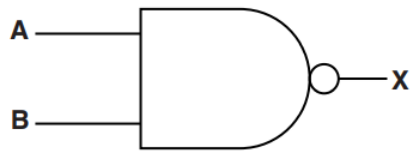
## Question 16


- 5 (a) Complete the truth table for this NAND gate:



A	B	X
0	0	
0	1	
1	0	
1	1	

[1]

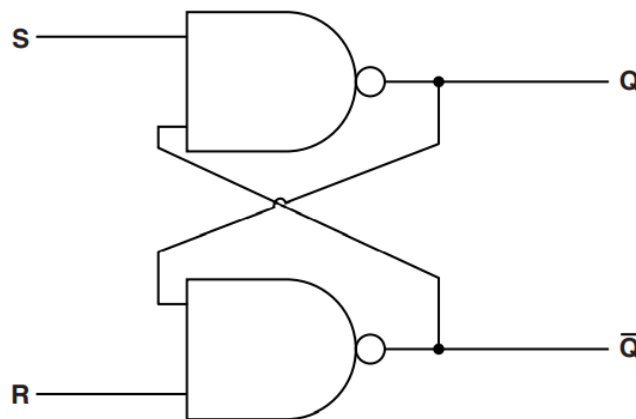A SR flip-flop is constructed using two NAND gates.



- (b) (i) Complete the truth table for the SR flip-flop.

	S	R	Q	$\bar{Q}$
Initially	1	0	0	1
R changed to 1	1	1		
S changed to 0	0	1		
S changed to 1	1	1		
S and R changed to 0	0	0		

[4]

- (ii) One of the combinations in the truth table should not be allowed to occur.

State the values of S and R that should not be allowed. Justify your choice.

S = ..... R = .....

.....

.....

.....

.....[3]

Another type of flip-flop is the JK flip-flop.

(c) (i) Give one extra input present in the JK flip-flop.

.....  
 .....[1]

(ii) Give **one** advantage of the JK flip-flop.


.....  
 .....[1]

(d) Describe the role of flip-flops in a computer.

.....  
 .....  
 .....  
 .....[2]
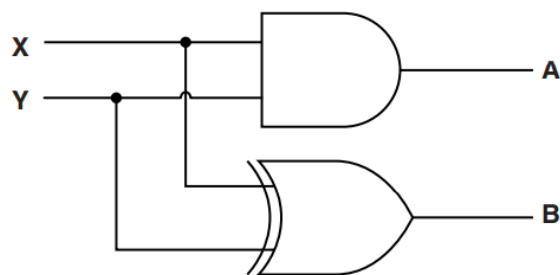
## Question 17

4 (a) (i) Complete the truth table for this logic circuit.



Input		Output	
X	Y	A	B
0	0		
0	1		
1	0		
1	1		

[2]

(ii) State the name given to this logic circuit.

..... [1]



(iii) Name the labels usually given to **A** and **B**.


Label **A** .....

Label **B** .....

Explain why your answers are more appropriate for the **A** and **B** labels.

.....  
.....  
.....  
..... [4]

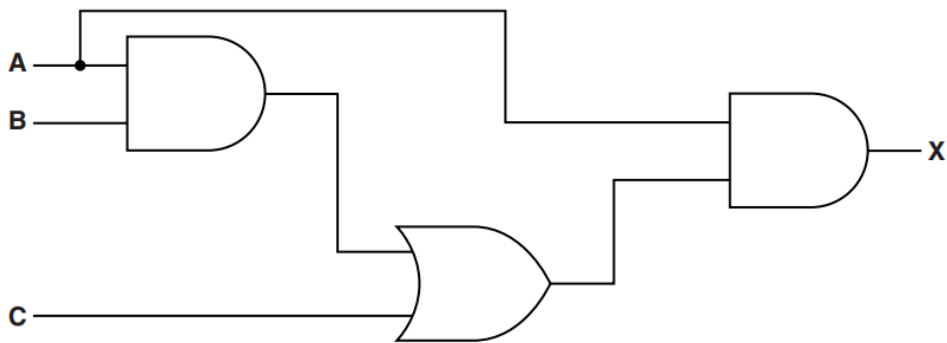(b) (i) Write the Boolean expression corresponding to the following logic circuit:



..... [2]

(ii) Use Boolean algebra to simplify the expression that you gave in **part (b)(i)**.

Show your working.


.....  
.....  
.....  
.....  
.....  
..... [3]

## Question 18

- 5 (a) (i) A half adder is a logic circuit with the following truth table.

Input		Output	
X	Y	A	B
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

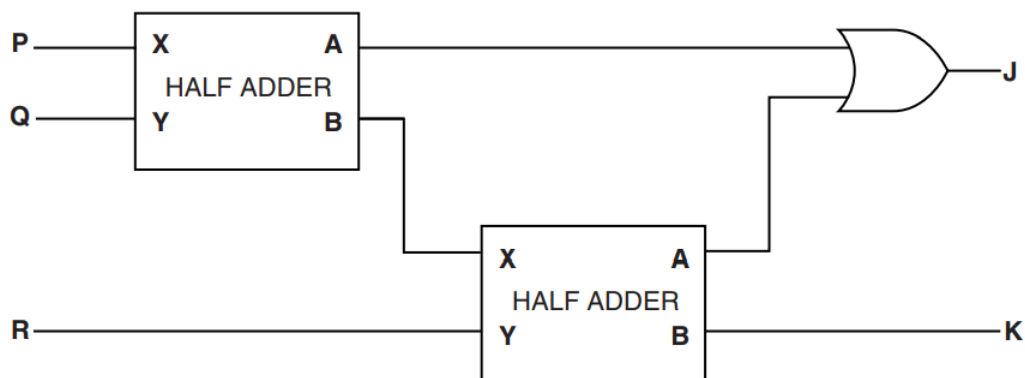The following logic circuit is constructed.



Complete the following truth table for this logic circuit.

Input			Working space	Output	
P	Q	R		J	K
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

[2]

- (ii) State the name given to this logic circuit.

..... [1]

(iii) Name the labels usually given to **J** and **K**.

Label **J** .....

Label **K** .....

Explain why your answers are appropriate labels for these outputs.


.....

.....

.....

..... [4]

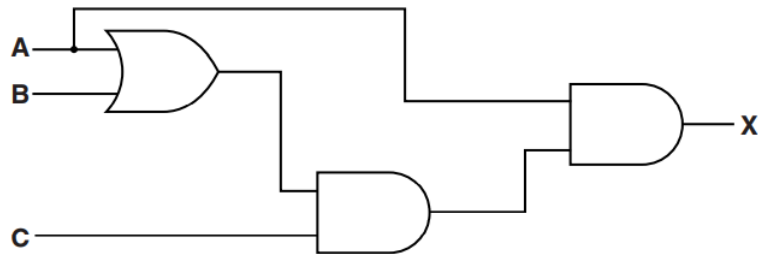(b) (i) Write down the Boolean expression corresponding to the following logic circuit:



..... [2]

(ii) Use Boolean algebra to simplify the expression given in **part (b)(i)**.

Show your working.

.....

.....

.....


.....

.....

..... [4]
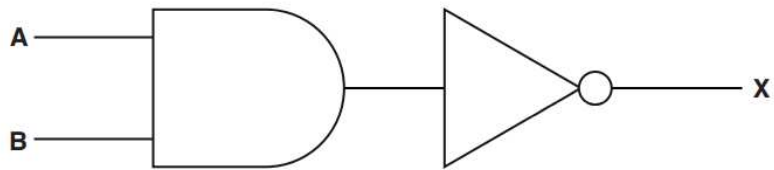
## Question 19


4 (a) (i) Complete the truth table for this logic circuit:



A	B	Working space	X
0	0		
0	1		
1	0		
1	1		

[1]

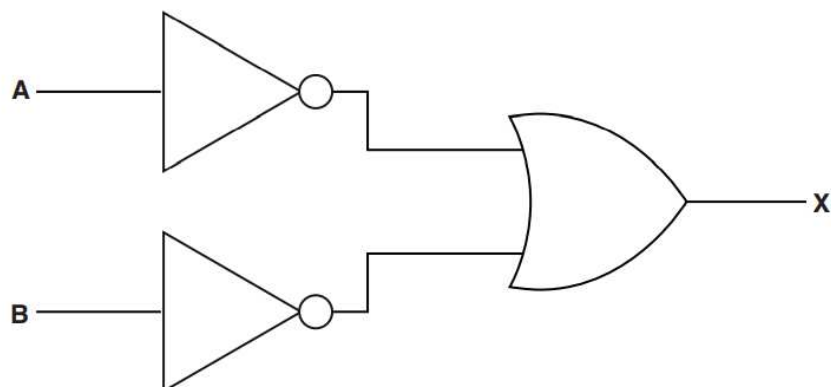(ii) Complete the truth table for this logic circuit:



A	B	Working space	X
0	0		
0	1		
1	0		
1	1		

[1]

**(b)** A student decides to write an equation for **X** to represent the full behaviour of each logic circuit.

**(i)** Write the Boolean expression that will complete the required equation for **X** for each circuit:


Circuit 1: **X** = .....

Circuit 2: **X** = .....[2]

**(ii)** Write the De Morgan's Law which is shown by your answers to **part (a)** and **part (b)(i)**.

.....[1]

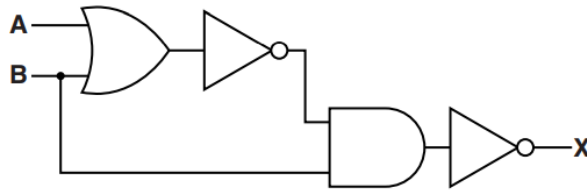**(c)** Write the Boolean algebraic expression corresponding to the following logic circuit:



.....[3]

**(d)** Using De Morgan's laws and Boolean algebra, simplify your answer to **part (c)**.

Show all your working.

.....

.....

.....

.....

.....

.....

.....[3]

## Question 20

- 5 (a) (i) Complete the Boolean function that corresponds to the following truth table.

INPUT			OUTPUT
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$X = \bar{A} \cdot B \cdot C + \dots\dots\dots [3]$$

The part to the right of the equals sign is known as the sum-of-products.

- (ii) For the truth table above complete the Karnaugh Map (K-map).

		AB			
		00	01	11	10
C	0				
	1				

[1]

The K-map can be used to simplify the function in **part(a)(i)**.

- (iii) Draw loop(s) around appropriate groups of 1's to produce an optimal sum-of-products. [2]

- (iv) Using your answer to **part (a)(iii)**, write the simplified sum-of-products Boolean function.

$$X = \dots\dots\dots [2]$$

(b) The truth table for a logic circuit with four inputs is given below:

INPUT				OUTPUT
A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

(i) Complete the K-map corresponding to the truth table above.

		AB			
CD					

[4]

(ii) Draw loop(s) around appropriate groups of 1's to produce an optimal sum-of-products.  
[2]

(iii) Using your answer to **part (b)(ii)**, write the simplified sum-of-products Boolean function.

X = .....[2]

## Question 21

- 5 (a) (i) Complete the Boolean function that corresponds to the following truth table.

INPUT			OUTPUT
P	Q	R	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

$$Z = P \cdot \bar{Q} \cdot \bar{R} + \dots\dots\dots[3]$$

The part to the right of the equals sign is known as the sum-of-products.

- (ii) For the truth table above complete the Karnaugh Map (K-map).

		PQ			
		00	01	11	10
R	0				
	1				

[1]

The K-map can be used to simplify the function in **part(a)(i)**.

- (iii) Draw loop(s) around appropriate groups of 1's to produce an optimal sum-of-products.  
[2]

- (iv) Using your answer to **part (a)(iii)**, write the simplified sum-of-products Boolean function.

$$Z = \dots\dots\dots[1]$$



(b) The truth table for a logic circuit with four inputs is given below:

INPUT				OUTPUT
P	Q	R	S	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

(i) Complete the K-map corresponding to the truth table above.

		PQ			
RS	00				
	01				
	11				
	10				

[4]

(ii) Draw loop(s) around appropriate groups of 1's to produce an optimal sum-of-products. [2]

(iii) Using your answer to **part (b)(ii)**, write the simplified sum-of-products Boolean function.

Z = .....[2]