




## ANSWERS LOGIC GATE

### Answer 1


Question	Answer	Marks																																													
5(a)	<div>1 mark for each pair of correct answers (shaded)</div> <table><thead><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></tbody></table>	A	B	C	Working space	X	0	0	0		0	0	0	1		1	0	1	0		1	0	1	1		0	1	0	0		1	1	0	1		1	1	1	0		0	1	1	1		0	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		0																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		0																																											
1	1	1		0																																											



Question	Answer	Marks																																		
5(b)	<b>1 mark</b> for name, <b>1 mark</b> for symbol, <b>1 mark</b> for truth table <ul style="list-style-type: none"> <li>NAND   </li> </ul> <table border="1" style="margin-top: 10px; width: 100%;"> <thead> <tr> <th colspan="2">Input</th><th rowspan="2">Output</th></tr> <tr> <th>A</th><th>B</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table> <ul style="list-style-type: none"> <li>NOR   </li> </ul> <table border="1" style="margin-top: 10px; width: 100%;"> <thead> <tr> <th colspan="2">Input</th><th rowspan="2">Output</th></tr> <tr> <th>A</th><th>B</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	Input		Output	A	B	0	0	1	0	1	1	1	0	1	1	1	0	Input		Output	A	B	0	0	1	0	1	0	1	0	0	1	1	0	<b>3</b>
Input		Output																																		
A	B																																			
0	0	1																																		
0	1	1																																		
1	0	1																																		
1	1	0																																		
Input		Output																																		
A	B																																			
0	0	1																																		
0	1	0																																		
1	0	0																																		
1	1	0																																		

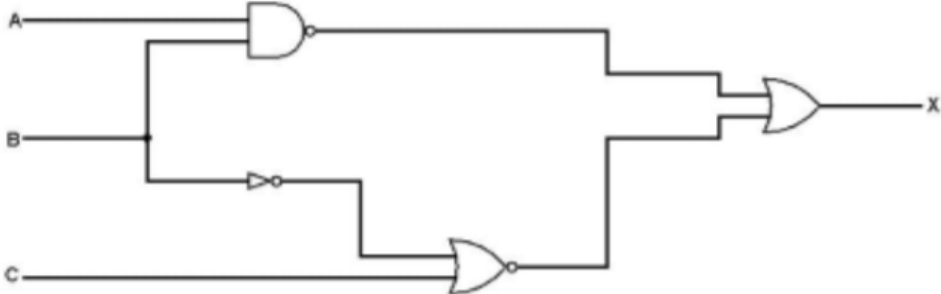Answer 2



Question	Answer	Marks
3	<p><b>1 mark</b> for each correct gate</p> <p><math>X = \text{NOT } (A \text{ AND } B) \text{ OR NOT } (\text{NOT } B \text{ OR } C)</math></p> 	4
4(a)(i)	<p><b>1 mark</b> only e.g.</p> <ul style="list-style-type: none"><li>• Read about the languages she will be using</li><li>• Visits the office prior to starting</li><li>• Speaks to her manager about concerns</li></ul>	1

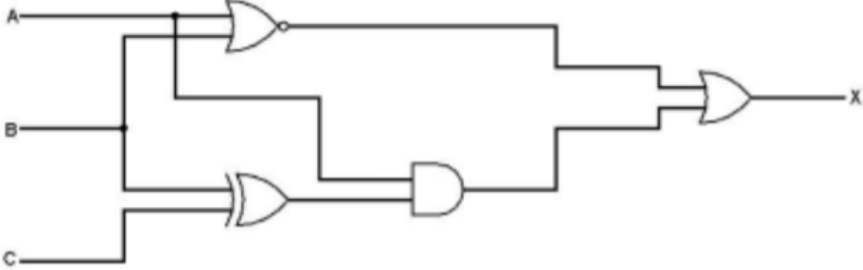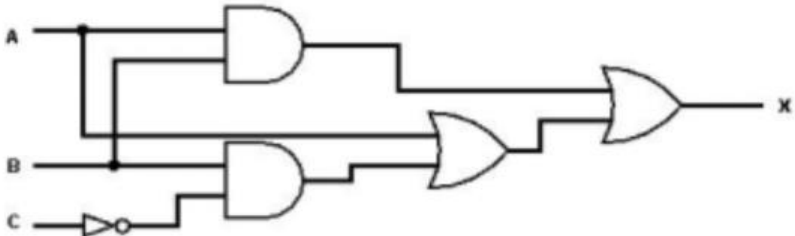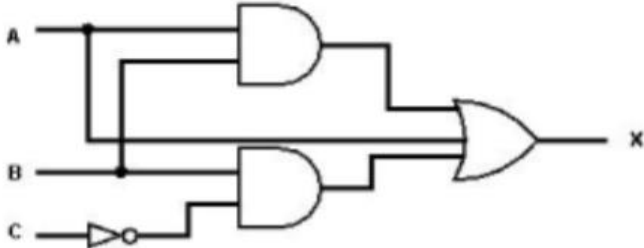Answer 3

Question	Answer	Marks
3(a)	<p><b>1 mark</b> per correct gate</p> <ul style="list-style-type: none"><li>• A NOR B</li><li>• B XOR C</li><li>• A AND (B XOR C)</li><li>• Final OR</li></ul> 	4


Question	Answer	Marks																																													
3(b)	<p><b>1 mark</b> for each correct pair of answers (4 shaded sections)</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working Space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>	A	B	C	Working Space	X	0	0	0		1	0	0	1		1	0	1	0		0	0	1	1		0	1	0	0		0	1	0	1		1	1	1	0		1	1	1	1		0	4
A	B	C	Working Space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		0																																											
0	1	1		0																																											
1	0	0		0																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		0																																											
3(c)	<p><b>1 mark</b> for name, <b>1 mark</b> for symbol matching the name</p> <p>NAND </p> <p>NOR </p>	2																																													

#### Answer 4

Question	Answer	Marks
6(a)	<p><b>1 mark</b> per gate      The OR gates may be re-sequenced</p>  <p>Alternatively: 3-input OR gate  <b>1 mark</b> for first three gates, and <b>2 marks</b> for 3-input OR gate</p> 	5

Question	Answer	Marks																																													
6(b)	<b>1 mark</b> for each pair of rows (shaded)	<b>4</b>																																													
	<table><tr><th>A</th><th>B</th><th>C</th><th>Working Space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>		A	B	C	Working Space	X	0	0	0		0	0	0	1		0	0	1	0		1	0	1	1		0	1	0	0		1	1	0	1		1	1	1	0		1	1	1	1		1
	A		B	C	Working Space	X																																									
	0		0	0		0																																									
	0		0	1		0																																									
	0		1	0		1																																									
	0		1	1		0																																									
	1		0	0		1																																									
	1		0	1		1																																									
	1		1	0		1																																									
	1		1	1		1																																									

Answer 5

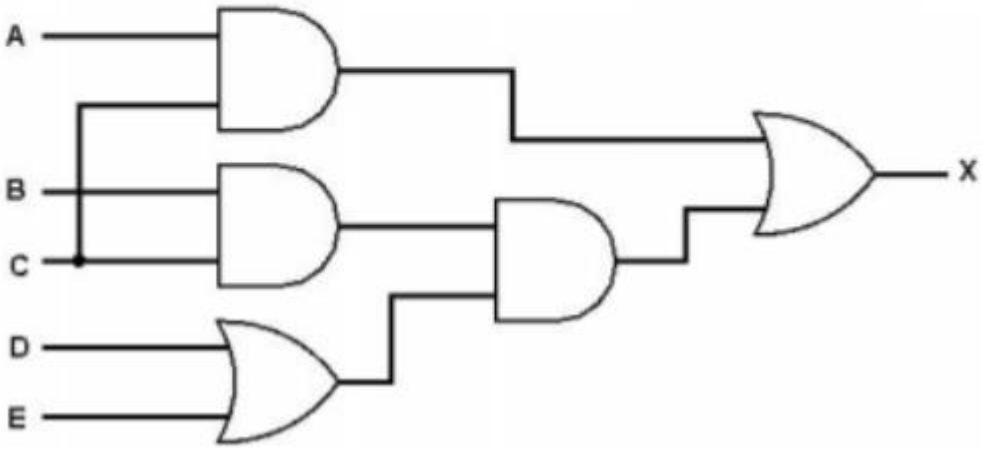Question	Answer	Marks
3(a)	<div>1 mark for each gate</div> <div><ul style="list-style-type: none"><li>• A AND C</li><li>• B AND C</li><li>• D OR E</li><li>• (B AND C) AND (D OR E)</li><li>• Final OR</li></ul></div> <div></div>	5


Question	Answer	Marks																																													
3(b)	<p><b>1 mark</b> for each pair of correct rows</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		0	0	0	1		1	0	1	0		1	0	1	1		0	1	0	0		0	1	0	1		1	1	1	0		0	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		0																																											
1	0	0		0																																											
1	0	1		1																																											
1	1	0		0																																											
1	1	1		1																																											

## Answer 6


Question	Answer	Marks
2(a)	<p><b>1 mark</b> per gate</p>	4

2(b)	1 mark for each pair of answers	4																																													
<table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>			A	B	C	Working space	X	0	0	0		1	0	0	1		1	0	1	0		1	0	1	1		1	1	0	0		1	1	0	1		1	1	1	0		1	1	1	1		0
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		0																																											

Answer 7

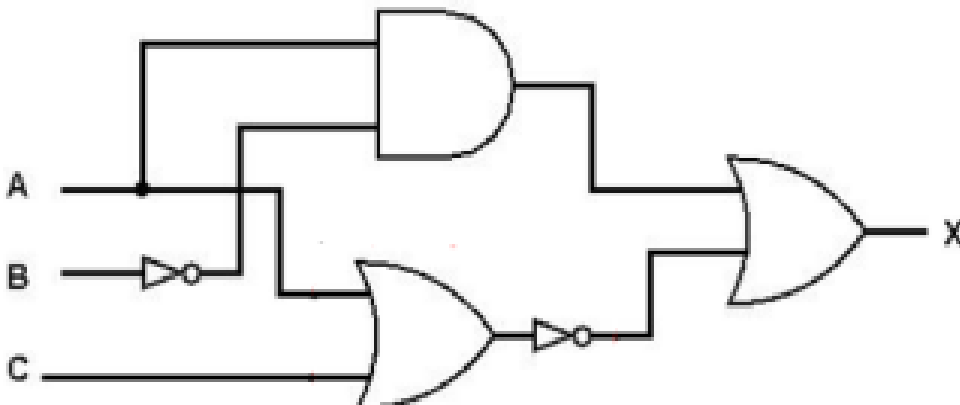Question	Answer	Marks																																													
5(a)	<p><b>1 mark</b> for each correct gate</p> <ul style="list-style-type: none"><li>• <b>A OR C</b></li><li>• <b>NOT(A OR C)</b></li><li>• <b>NOT B</b></li><li>• <b>A AND NOT B</b></li><li>• <b>Final OR</b></li></ul> 	5																																													
5(b)	<p><b>1 mark</b> for each pair of rows</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		0	0	1	0		1	0	1	1		0	1	0	0		1	1	0	1		1	1	1	0		0	1	1	1		0	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		0																																											
0	1	0		1																																											
0	1	1		0																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		0																																											
1	1	1		0																																											

Answer 8

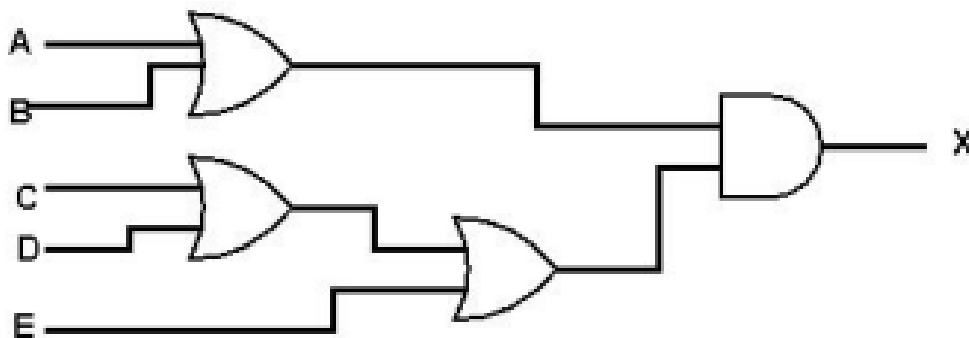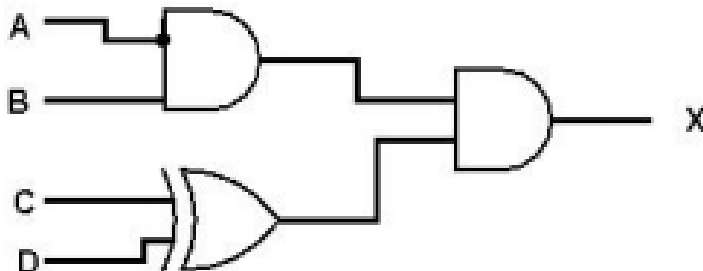
Question	Answer	Marks																																													
4(a)	<p>1 mark per bullet:</p> <ul style="list-style-type: none"><li>• A OR B</li><li>• C OR D OR E</li><li>• Final AND</li></ul> 	3																																													
4(b)	<p>1 mark for each correct pair of rows</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		0	0	0	1		1	0	1	0		1	0	1	1		0	1	0	0		1	1	0	1		1	1	1	0		1	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		0																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		1																																											

Answer 9

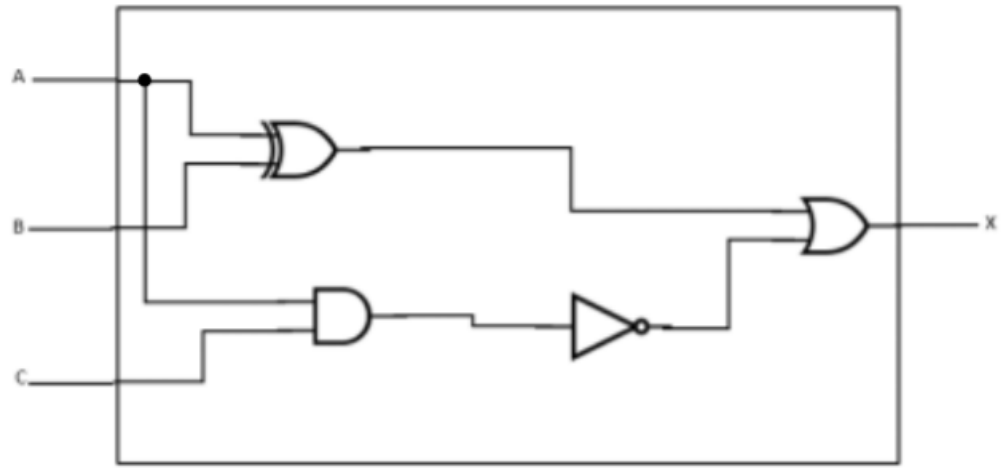
Question	Answer	Marks																																													
2(a)	<p><b>1 mark</b> for each gate with the correct inputs. Final two gates must also have the correct output.</p> <pre>graph LR     H --&gt; NOT1[NOT]     NOT1 --&gt; OR1[OR]     D --&gt; AND1[AND]     T --&gt; NOT2[NOT]     W --&gt; NOT3[NOT]     NOT2 --&gt; AND2[AND]     NOT3 --&gt; AND2     AND1 --&gt; OR1     AND2 --&gt; OR1     OR1 --&gt; X     AND2 --&gt; Y</pre>	6																																													
2(b)	<p><b>One mark</b> for each pair of rows.</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		1	0	1	0		1	0	1	1		0	1	0	0		0	1	0	1		0	1	1	0		0	1	1	1		0	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		0																																											
1	0	0		0																																											
1	0	1		0																																											
1	1	0		0																																											
1	1	1		0																																											



Answer 10

Question	Answer	Marks																																													
5(a)	<p>1 mark per correct gate with correct inputs</p> 	3																																													
5(b)	<p>1 mark for each correct pair of lines</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>	A	B	C	Working space	X	0	0	0		0	0	0	1		0	0	1	0		1	0	1	1		0	1	0	0		1	1	0	1		0	1	1	0		0	1	1	1		0	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		0																																											
0	1	0		1																																											
0	1	1		0																																											
1	0	0		1																																											
1	0	1		0																																											
1	1	0		0																																											
1	1	1		0																																											


Answer 11

Question	Answer	Marks
8(a)	<p><b>1 mark</b> for each logic gate with the correct inputs</p> 	4

Question	Answer	Marks																																													
8(b)	<p>One mark for each correct pair of lines</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working Space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>	A	B	C	Working Space	X	0	0	0		1	0	0	1		1	0	1	0		1	0	1	1		1	1	0	0		1	1	0	1		1	1	1	0		1	1	1	1		0	4
A	B	C	Working Space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		0																																											

Answer 12

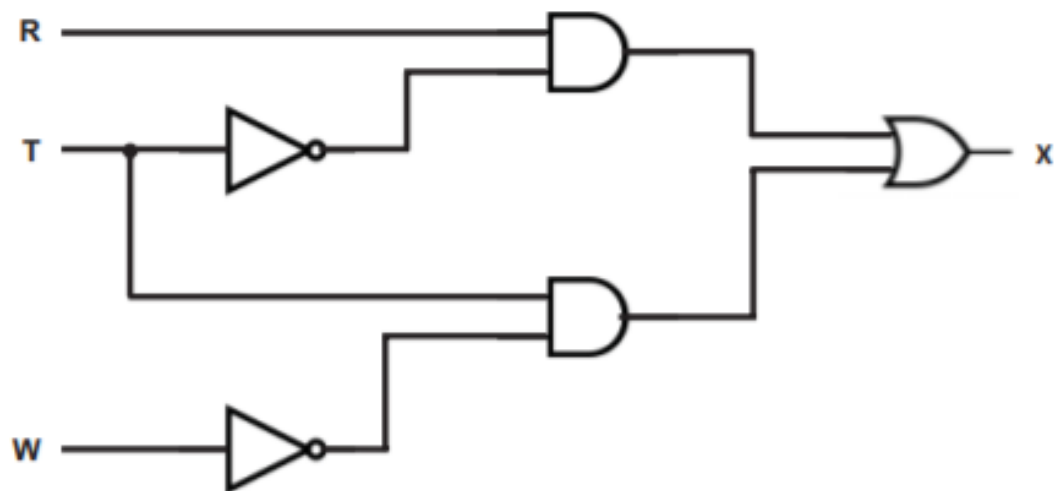5 (a) (i) One mark for each correct gate.



[5]

(ii)  $\underline{(R.\bar{T})} + \underline{(T.\bar{W})}$  // (R AND NOT T) OR (T AND NOT W)

[2]


(iii) One mark for each pair of lines as shaded.

INPUT			Working space	OUTPUT X
R	T	W		
0	0	0		0
0	0	1		0
0	1	0		1
0	1	1		0
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		0

[4]

Answer 13

1 (a) ONE mark for each correct gate.

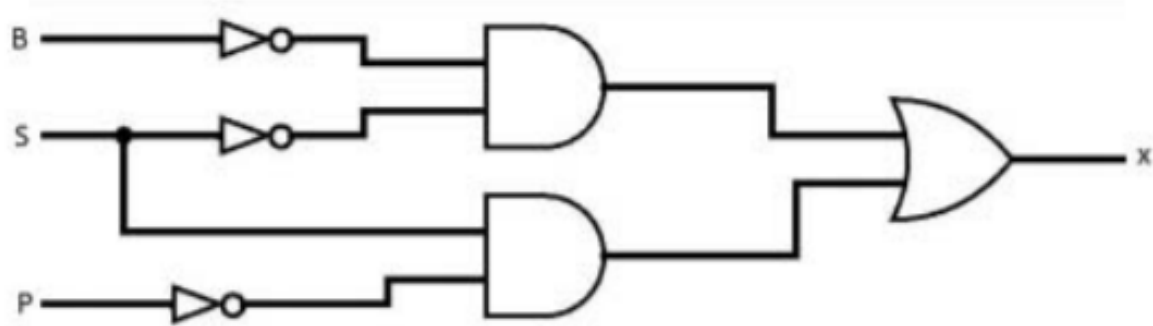

[6]


(b) ONE mark for each pair of rows.

B	S	P	Working space	X
0	0	0		1
0	0	1		1
0	1	0		1
0	1	1		0
1	0	0		0
1	0	1		0
1	1	0		1
1	1	1		0

[4]

Answer 14

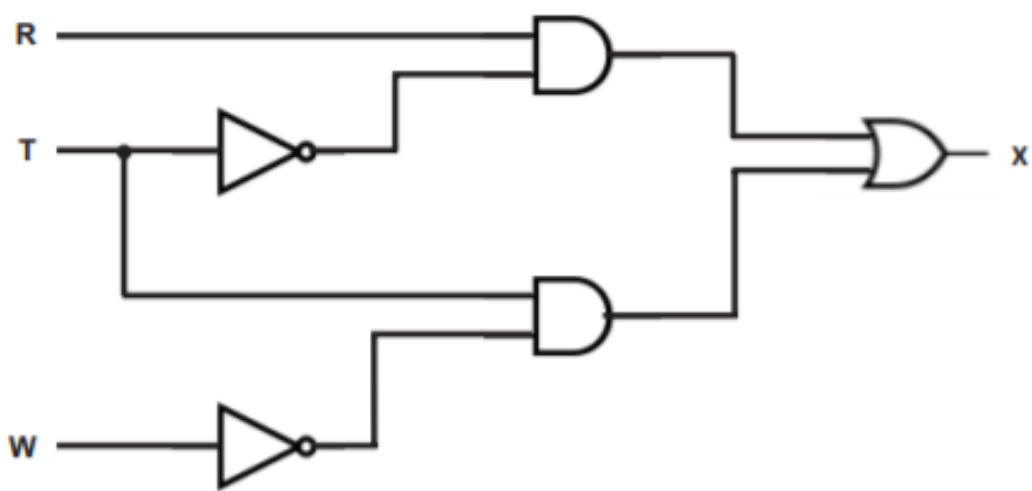5 (a) (i) One mark for each correct gate.



[5]

(ii)  $(R.\bar{T})+(T.\bar{W})$  // (R AND NOT T) OR (T AND NOT W)

[2]


(iii) One mark for each pair of lines as shaded.

INPUT			Working space	OUTPUT X
R	T	W		
0	0	0		0
0	0	1		0
0	1	0		1
0	1	1		0
1	0	0		1
1	0	1		1
1	1	0		1
1	1	1		0

[4]

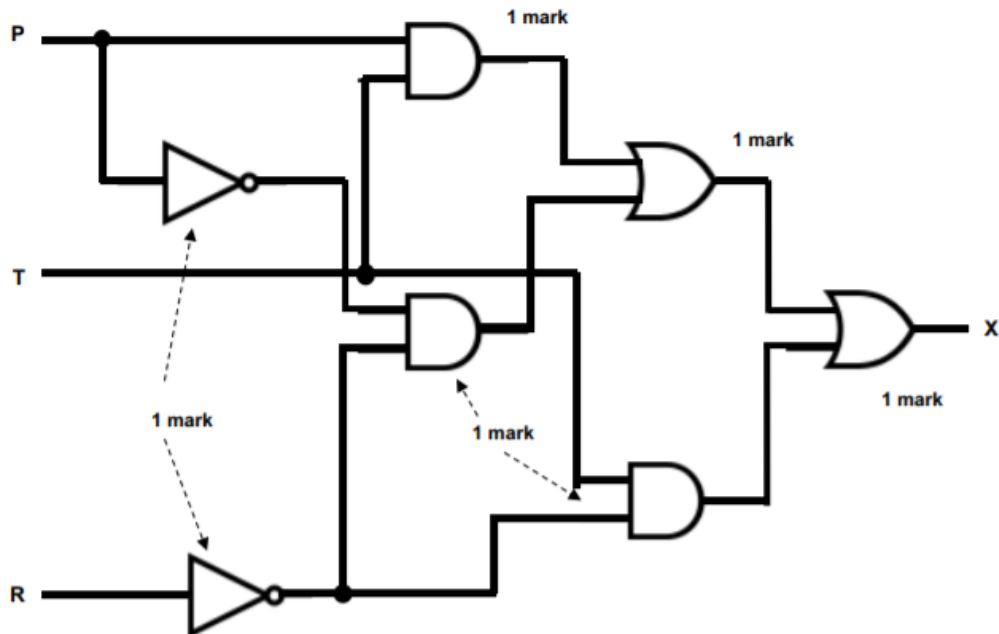
# Answer 15

7 (a) since it is possible to simplify the original conditions, at least 3 possible answers exist for the logic circuit.




Note: input T has 2 cross overs that should not be connections

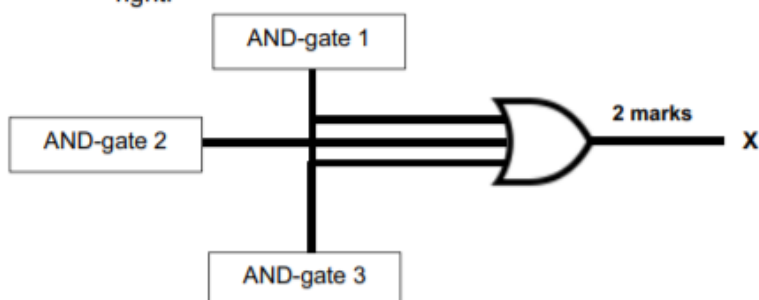
Note: it is possible to use a 3-input OR gate rather than the two 2-input OR gates on the top right:



Alternative solution 1:

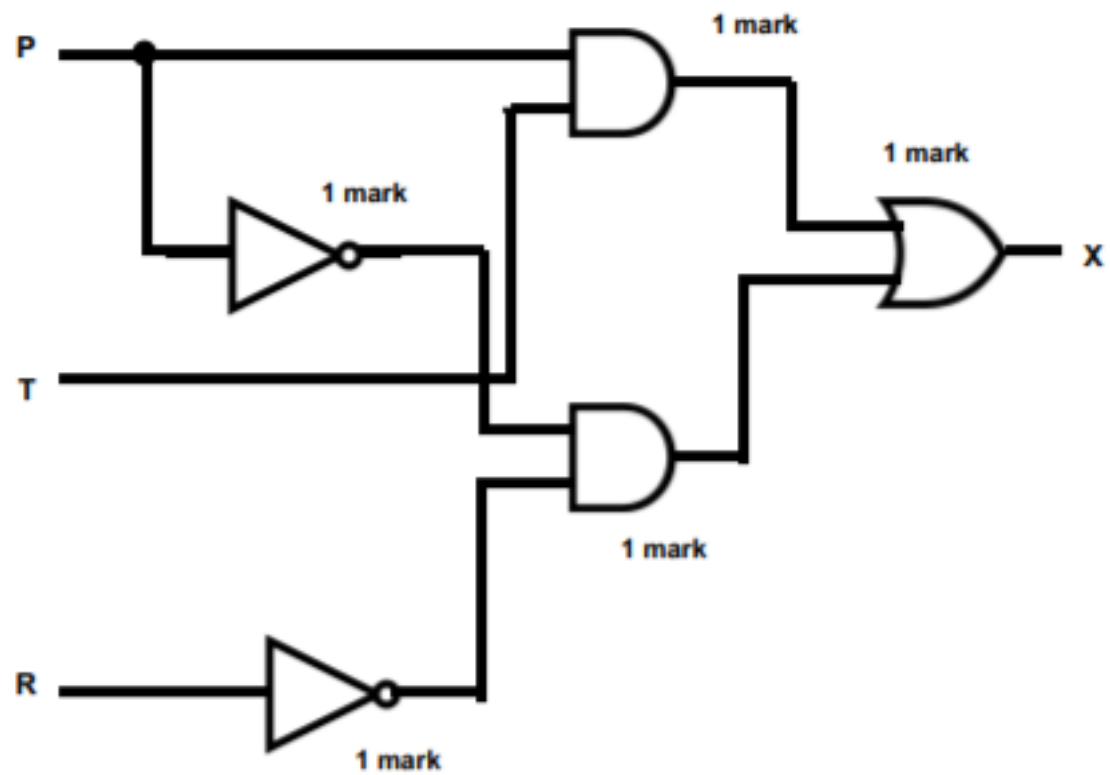

Alternative solution 2:

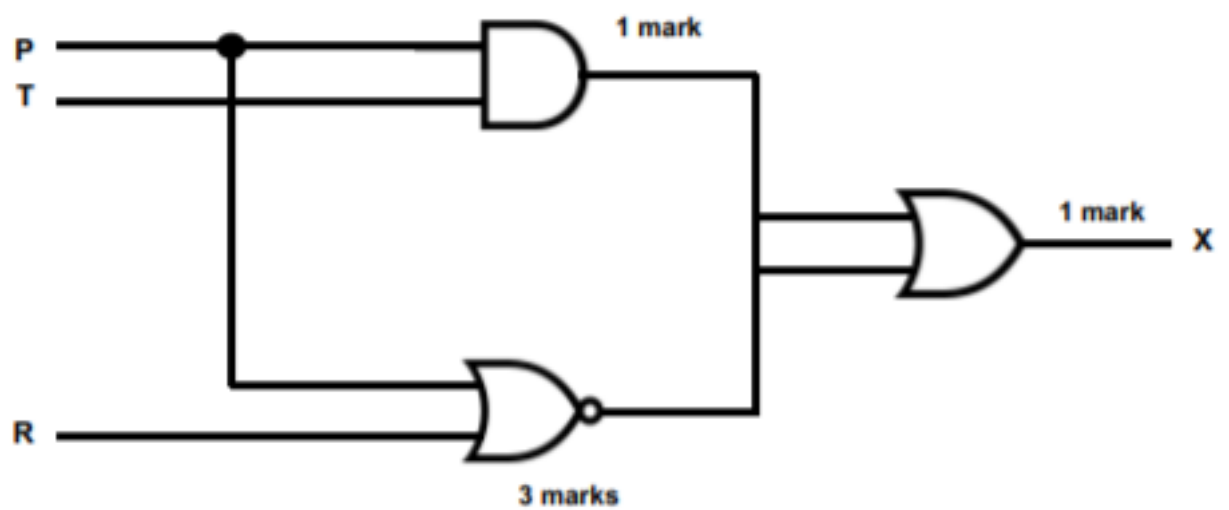

(b)

P	T	R	Workspace	X
0	0	0		1
0	0	1		0
0	1	0		1
0	1	1		0
1	0	0		0
1	0	1		0
1	1	0		1
1	1	1		1

} 1 mark

} 1 mark


} 1 mark

} 1 mark

[4]

Answer 16

6 (a)

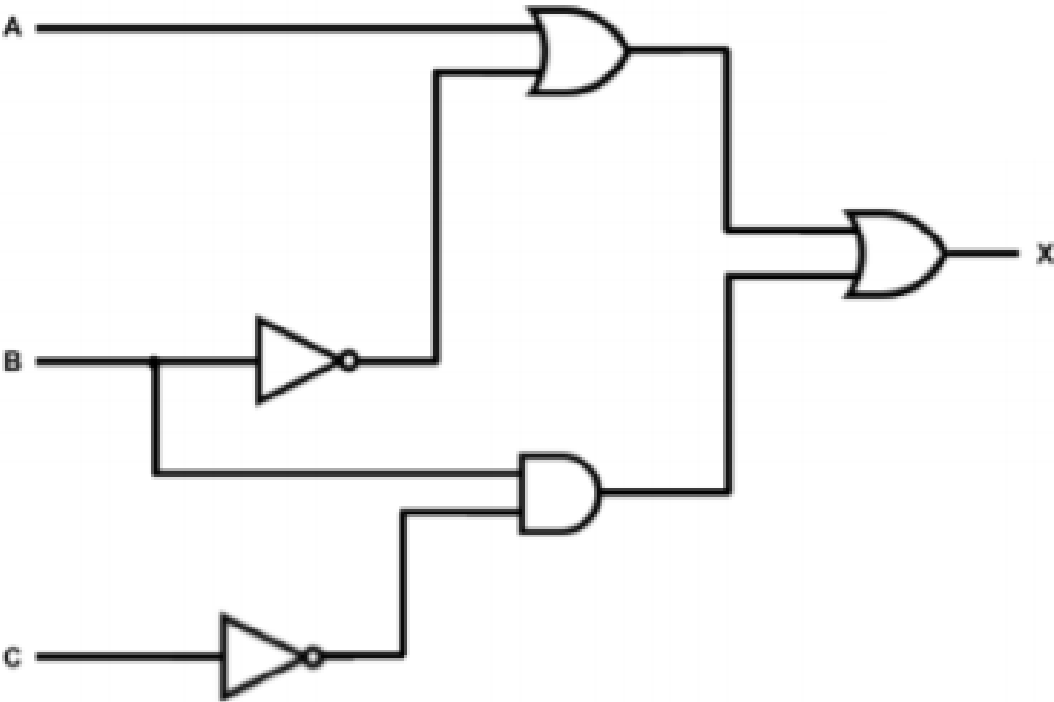

[5]



(b)

A	B	C	working	X	
0	0	0		1	} 1 mark
0	0	1		1	
0	1	0		1	} 1 mark
0	1	1		0	
1	0	0		1	} 1 mark
1	0	1		1	
1	1	0		1	} 1 mark
1	1	1		1	

[4]

(c) ((A is NOT 1 AND B is 1) OR (B is NOT 1 OR C is 1)) AND C is NOT 1

<----- 1 mark -----> <----- 1 mark -----> <----- 1 mark ----->

NOTE: all brackets may not be shown – but check answer still correct

Alternatives include:

((NOT A AND B) OR (NOT B OR C)) AND NOT C

$(\bar{A} \cdot B + (\bar{B} + C)) \cdot \bar{C}$

NOTE: expressions may be reversed but still OK


(e.g. NOT C AND ((NOT A AND B) OR (NOT B OR C))

NOT C AND ((NOT B OR C) OR (NOT A AND B)) and so on)

[3]

**Answer 17**


B	S	P	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

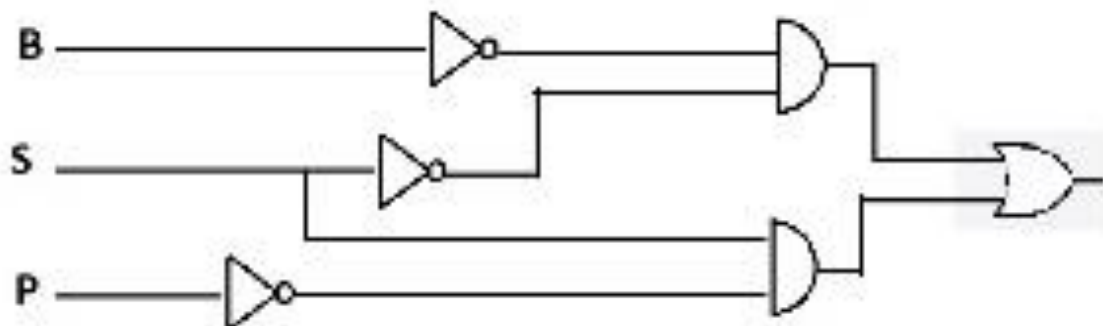

**Answer 18**


- 8 (a) 2 marks per part  
 IF candidate uses 2 gates mark from 2 gate diagram if draws 3 gates mark from 3 gate diagram for all 3 parts

(i) (allow correct alternatives)

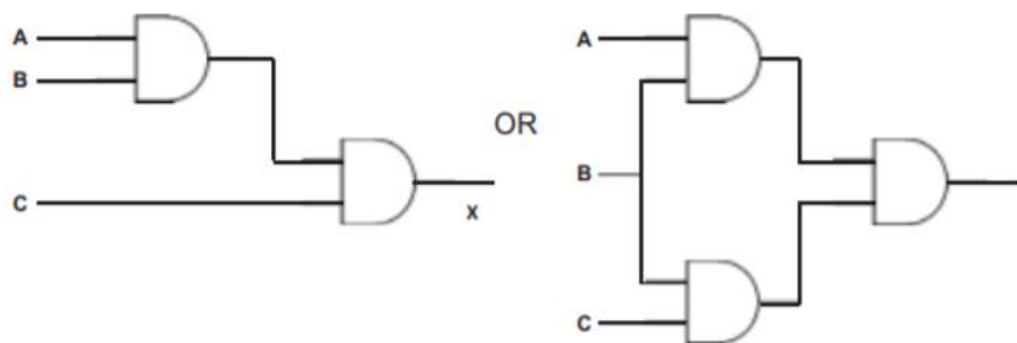


[2]

(ii)

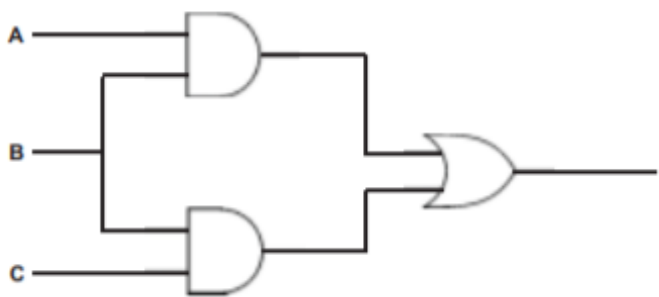

[2]

(iii) (allow correct alternatives)

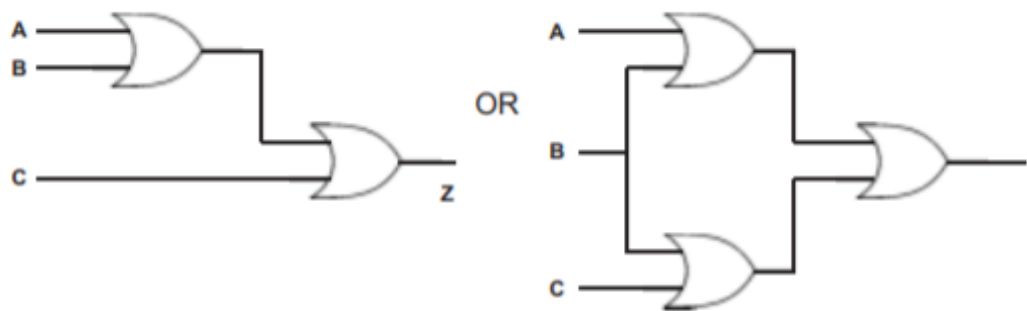

[2]

(b)

A	B	C	X	Y	Z
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	1	1
1	0	0	0	0	1
1	0	1	0	0	1
1	1	0	0	1	1
1	1	1	1	1	1

2 marks   2 marks   2 marks

(−1 mark for each error in each column)

[6]


Answer 19

8 (a)

A	B	C	X	
0	0	0	1	1 mark
0	0	1	1	
0	1	0	0	1 mark
0	1	1	0	
1	0	0	0	1 mark
1	0	1	1	
1	1	0	0	1 mark
1	1	1	0	

[4]

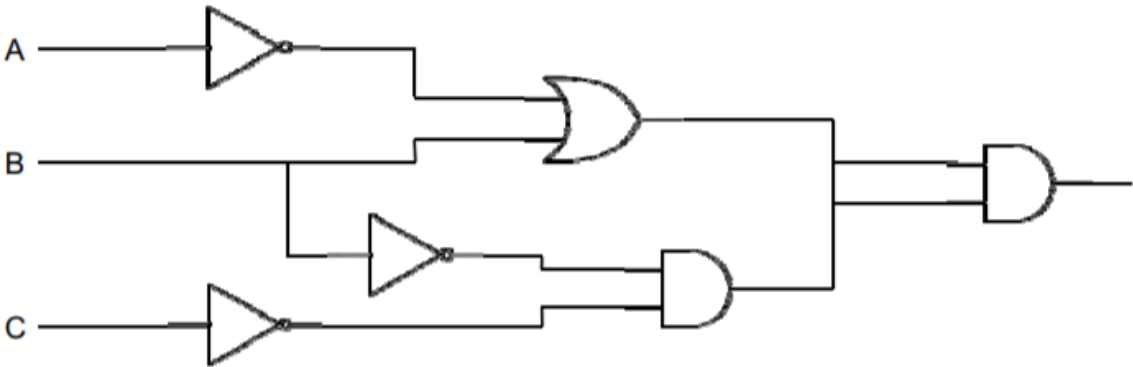
(b) 1 mark per correct logic gate in correct position



[6]

Answer 20

6 (a)

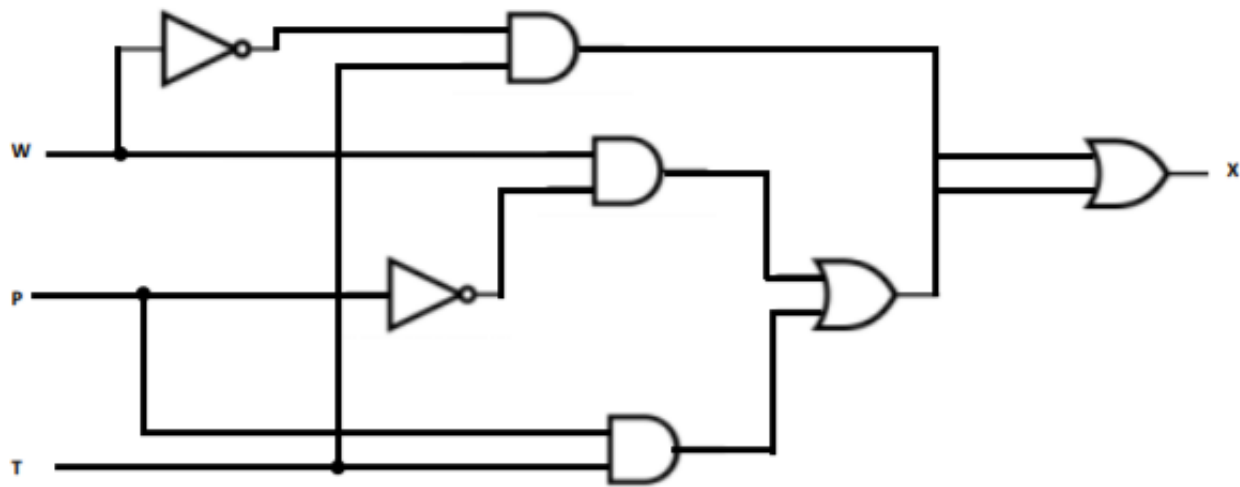

(corresponds to:  $[W = 1 \text{ AND } P = \text{NOT } 1] \text{ OR } [T = 1 \text{ AND } P = 1] \text{ OR } [W = \text{NOT } 1 \text{ AND } T = 1]$ )

1 mark for each correct logic gate in correct position –

[7]

(b)

input W	input P	input T	output X
0	0	0	<b>0</b>
0	0	1	<b>1</b>
0	1	0	<b>0</b>
0	1	1	<b>1</b>
1	0	0	<b>1</b>
1	0	1	<b>1</b>
1	1	0	<b>0</b>
1	1	1	<b>1</b>

1 mark

1 mark


1 mark

1 mark

[4]

Answer 21

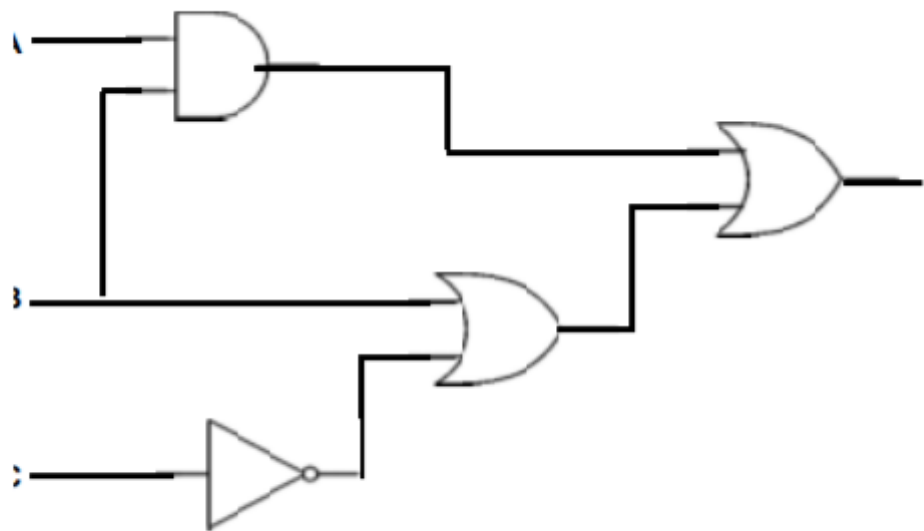9 (a) 1 mark for each correct logic gate (accept other logic gate nomenclature)



If a candidate has only one input to AND gate or an OR gate they lose the mark for that gate [4]


(b)

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

[4]

Answer 22

4 (a) 1 mark for each correct logic gate

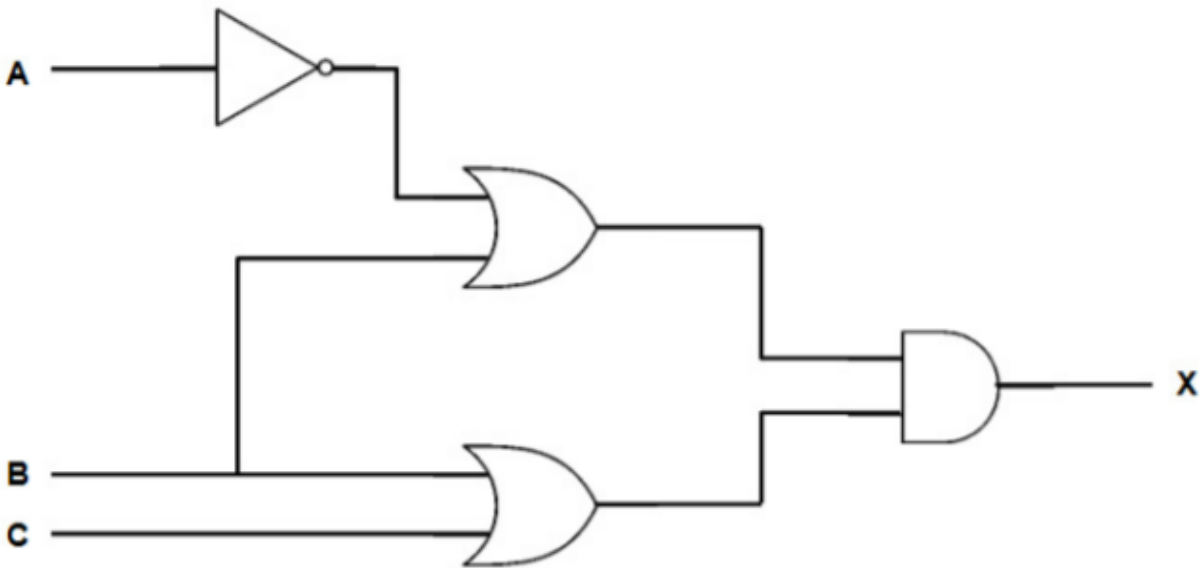

[4]

(b)

A	B	C	X	
0	0	0	0	} 1 mark
0	0	1	1	
0	1	0	1	} 1 mark
0	1	1	1	
1	0	0	0	} 1 mark
1	0	1	0	
1	1	0	1	} 1 mark
1	1	1	1	

[4]

**Answer 23**

**9 (a)**

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

(1 mark for the 1,0 and 1 mark for 0, 0)

[2]

**(b)**

A	B	C	D	Y
0	0	0	1	0
0	1	1	0	0
1	0	1	1	1
1	1	1	0	0

(1 mark for each row).

[4]